

**Name of the Examinations: B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR FIRST SEMESTER SUPPLEMENTARY EXAM - 2018**


**Subject : NETWORK SYNTHESIS**

**Time : 3 Hours**

**Full Marks :100**

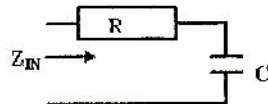**Answer any five questions All questions carry equal marks**

- 1(a) What is a PR function? From your definition prove that the input impedance function of the following circuit is PR



10

- 1(b) If  $Z_1(S)$  and  $Z_2(S)$  are PR functions then using your definition in part(a) prove that  
 (i)  $Z_1(S) + Z_2(S)$  is a PR function  
 (ii)  $1/Z_1(S)$  is a PR function.  
 (iii)  $Z_1(Z_2(S))$  is a PR function.

10

- 2(a) If  $P(S)$  is a strictly Hurwitz polynomial, show that  $\frac{P(S)}{P'(S)}$  is PR,

where  $P'(S) = \frac{dP(S)}{dS}$

10

- 2(b) If  $P(s)$  is a Hurwitz polynomial show that  $\phi(S) = \frac{M(S)}{N(S)}$  is a PR function where,  $M(s)$  is the even part of  $P(s)$  and  $N(s)$  is the odd part of  $P(s)$ .

10

- 3(a) Find the voltage transfer function of the circuit shown in Fig 1(a).

10

- 3(b) Find the input impedance of the circuit shown in Fig 1(b). Find the range of values of  $C_1$  such that the function remains PR.

10

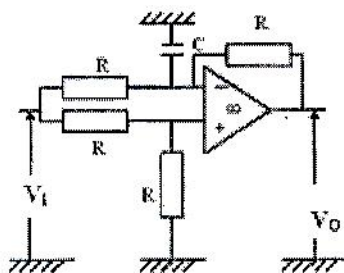


Fig 1(a)

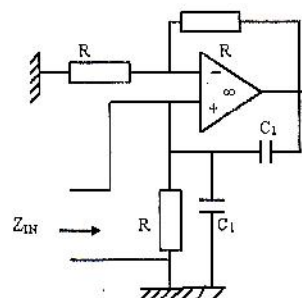


Fig 1(b)

- 4(a) Assume that  $Z(S)$  is a PR function and  $\text{Re}[Z(S)] = 0$ . Show that  $Z(S)$  can be expressed either as  $\frac{M(S)}{N(S)}$  or as  $\frac{N(S)}{M(S)}$  where  $M(S)$  and  $N(S)$  respectively represent even and odd polynomials in  $S$ .

10

- 4(b) From the result proved in part (a) obtain the general expression for an LC driving point impedance function. Hence derive the Foster I and Foster II realization technique for LC impedance function. Find the Foster I and Foster II realization for the following LC function

$$Z_{LC}(S) = \frac{S(S^2 + 2)}{(S^2 + 1)(S^2 + 3)}$$

10

- 5(a) Show how a general expression of  $Z_{RC}(S)$  may be derived from the general expression of  $Z_{LC}(S)$

10

- 5(b) Starting from the general expression of  $Z_{LC}(s)$  show that  $Z_{RC}(S)$  can have a pole at  $S=0$  and cannot have a zero at  $S = 0$ .

10

- 5(c) Obtain two Cauer realizations for the following RC driving point admittance function.

$$Y_{RC}(S) = \frac{S(S + 3)}{(S+1)(S + 4)}$$

10

- 6(a) Derive the expression for  $L$  and  $C$  used in a constant  $K$  low pass filter in terms of its cut off frequency and the  $Z_1 Z_2$  product. Also find the expression for the phase shift in the pass band.

10

- 6(b) What are the disadvantages of the above filter? Show how these disadvantages may be overcome in an  $m$ -derived filter. Find the expression for  $m$  and  $f_\infty$  for such filter.

10

- 7(a) Derive the expression  $\sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{Z_2}}$  for a symmetric T network. Assume the usual meanings of the symbols used.

10

- 7(b) Show how the general filter characteristics of a reactance T network may be predicted using the above expression.

- 8 Design a state variable band pass filter described by the following voltage transfer function

20

$$\frac{V_o(S)}{V_i(S)} = \frac{\omega_o S}{S^2 + a\omega_o S + \omega_o^2}$$

where,  $\omega_o = 1000$  rad/sec and  $a = 0.1$