

B.ETCE 2nd yr. Examination 2018
First Semester (**Supplementary**)

DIGITAL LOGIC CIRCUITS

Time: 3 hours

Full Marks : 100

Answer any *five* questions
All questions carry equal marks

1. (a) Obtain the maxterm and minterm representations of the following Boolean function.

$$f(A, B, C) = A + B + A' C$$

- (b) Obtain the simplified expression for the following Boolean function using K-map.

$$f(A, B, C, D) = \Sigma (0, 2, 5, 7, 8, 10, 13, 15)$$

2. (a) Design a 8:1 Multiplexer using 2:1 MUX units and explain its working principle.

- (b) Realize the following Boolean function using a 4:1 multiplexer and other SSI gates if necessary.

$$f(A, B, C) = AB + BC + AC$$

3. (a) Design a 3-bit binary adder and explain its working principle.

- (b) Realize the following functions using a decoder and minimum number of SSI gates.

$$F_1(A, B, C) = A' B + A C$$

$$F_2(A, B, C) = A B + A' C$$

[Turn over

4. (a) Design a 6-bit magnitude comparator circuit using one 7485 IC and other SSI gates if required and explain the design steps.
(b) Design a 11-bit parity checker circuit using one 74180 IC and other SSI gates if required and explain the design steps.
5. (a) Draw the circuit diagram of a JK flip-flop using NAND gates only, explain its operation and hence obtain the truth table.
(b) Convert a D flip-flop into a JK flip-flop. Obtain an expression for f_{\max} of the resulting circuit.
6. (a) Design a 4-bit buffer register with appropriate control line and explain its operation.
(b) Design a 4-bit ring counter and explain its operation with the help of a timing diagram. Mention the advantages and disadvantages of a ring counter.
7. (a) Design a mod-5 ripple counter using JK flip-flops. Consider low active CLR lines for your design. How will you modify the design if low active PRESET lines are available?
(b) Design a mod-5 synchronous up / down counter using JK flip-flops.