

B. ETCE 3RD YEAR 2ND SEMESTER EXAMINATION-2018

Subject: IC DESIGN

Time: 3 Hours

Full Marks: 100

All parts of the same question must be answered at one place only

Model parameters for NMOS and PMOS device

Parameters	NMOS	PMOS
L_{min}	180nm	180nm
W_{min}	240nm	240nm
V_{th}	0.7V	-0.8V
λ (V ⁻¹)	0.1	0.2
μ (cm ² /Vs)	350	100
C_{ox} (fF/ μ m ²)	6	6

PART-I

1. Answer any Five Questions: [Marks: 5×8=40]
- A) What is sub threshold conduction? Why MOS in sub threshold produces higher gain than MOS in saturation (*Explain with $\log(I_D)$ - V_{GS} plot*)?
 - B) What is channel length modulation effect? How the voltage current characteristics are affected because of this effect?
 - C) What is trans-conductance (g_m) of a MOS transistor? Plnt g_m - V_{GS} with V_{DS} as a parameter and g_m - V_{DS} with V_{GS} as a parameter.
 - D) Draw the ideal characteristics of a CMOS inverter and explain the different parts of the characteristic based on the operation point of those MOSFETs.
 - E) How body bias changes the threshold voltage of a MOSFET? Explain with diagram.
 - F) Explain why the structures shown below cannot operate as a current source even though the transistors are in saturation.

 


Figure 1

- G) What is delta delay in VHDL? How Transport and inertial delays are described?

[Turn over

PART-II
(Compulsory)

2. **Design** one cascode current mirror with output resistance not less than $1\text{ M}\Omega$. Find the **maximum voltage variation** at the output node of the current mirror.

OR

Design one cascode amplifier with resistive load for a voltage gain more than 100. Find the **maximum voltage variation** at the output node of the amplifier. [Marks =20]

PART-III
(Answer any Two)

3. Find the gain expressions of the amplifier circuits shown below. [Marks: $2 \times 10 = 20$]
A) Consider $\lambda \neq 0$ and $\gamma \neq 0$.

 


Figure 2

- B) Consider $\lambda \neq 0$ and $\gamma = 0$.

 


Figure 3

4. Find I_x vs V_x plot of the circuit shown below when V_x is varied from 0V to V_{DD} . Specify the voltage ranges corresponding to different transistor operating region. [Marks: 14+6 =20]
(Consider supply voltage $V_{DD}=3V$, $I_1=1\mu A$ (ideal), $V_{THN}=0.7V$ and $K = \mu C_{ox}W/L = 200 \mu A/V^2$ and $R_1 = 20K\Omega$)

 


Figure 4

5. A) The circuit shown in Figure 2 has following characteristics: $V_{th}=2V$, $I_1=1\mu A$ (ideal), $V_{THN}=0.7V$ and $K = \mu C_{ox}W/L = 200 \mu A/V^2$ with $V_{BODY} = 0V$. If the initial voltage on the capacitor is 3V, plot V_x with respect to time. (keep in mind that body to source conduction starts if $V_{SD} \leq -0.7V$ because of forward bias between body to source junction) [Marks: 12]

 


Figure 5

- B) Find the Voltage V_x plot of the circuit with respect to time. (Consider zero charge on the capacitor at time $t=0$). [Marks: 8]

 


Figure 6