

Bachelor of Instrumentation and Electronics Engineering, 2019
2nd year, 2nd semester
DIGITAL ELECTRONICS

Time : Three hours

Full Marks : 100

ALL MODULES ARE COMPULSORY.**Module – I (4 Marks)**

- Q1. (a) Convert $(408C1.D6)_{16}$ to base-4 system.
 (b) What are Self-Complementing BCD codes ? Give an example. (2+2)

Module – II (6 Marks)

- Q2. Perform the following arithmetic operations :
 (a) $(-39) + (-28)$ using 7-bit 2's complement number system.
 (b) $(9659) + (6738)$ using Normal BCD system. (3+3)

Module – III (40 Marks)**(Answer Any TWO from Q3, Q4 and Q5)**

- Q3. (a) Draw the p-MOS circuit which realizes the following function :

$$F(A, B, C) = A'C' + ABC$$
 (b) What logic function is realized by the circuit shown in Figure P3(b) ?
 (c) In Figure P3(c), a circuit is implemented using one 4:1 MUX. What is the function, F, available at its output in minimal form ?
 (d) Realize a two input XNOR function using only two 2:1 Multiplexers. (5 + 5 + 5 + 5)
- Q4. (a) Can we use the hypothetical logic Gate shown in Figure P4(a) as one Universal Logic Gate ? Explain.
 (b) In the circuit shown in Figure P4(b), if the output required is $F = A'B'C + A'B'D$, what type of gates are G1 and G2 ?
 (c) Using a suitable decoder and necessary OR-gates realize a full-subtractor. Use proper input and output signal names. (5 + 5 + 10)

- Q5. Using Quine-McCluskey's tabular method, obtain the minimized SOP realization for the function :

$$F(A, B, C, D) = \sum m(0, 1, 2, 7, 9, 13, 15) + d(8, 10, 14)$$

- (a) ignoring combinational hazard, and
 (b) removing combinational hazard.

(15 + 5)

Module – IV (50 Marks)

(Answer Q6 and Any TWO from Q7, Q8 and Q9)

- Q6. (a) In the circuit shown in Figure P6(a), the flip-flops have set-up time of 5 nSec and a worst case clock-to-output delay of 10 nSec. The AND gate has a delay of 5 nSec. What is the maximum possible clock rate for the circuit to operate faithfully ?
- (b) Find out the count sequence ($Q_2Q_1Q_0$) for the circuit shown in Figure P6(b). Assume initially all the three memory elements were in reset state.
- (c) The circuit shown in Figure P6(c), performs a certain function. Derive an expression for the next state Q_{n+1} in terms of X and previous state Q_n .

(5 + 10 + 5)

- Q7. (a) What is the "decoding spike problem" ? How can it be avoided ?
- (b) Using SR-flip flop as the memory element realize a sequential binary to gray code converter. The input binary bits are coming serially starting from the MSB.

(5 + 10)

- Q8. Realize a sequence detector circuit which produces a logic 1 output whenever it detects a sequence "110". The output is zero otherwise. Use T-Flip flops as the memory elements. Is there any lock-out possibility in your design ?

(14 + 1)

- Q9. Design a sequence generator which generates the sequence ... 100110... repeatedly. Use minimum number of D-Flip flops.

(15)

 


FIGURE P3(b)

 


FIGURE P3(c)

 


FIGURE P4(a)

 


FIGURE P4(b)

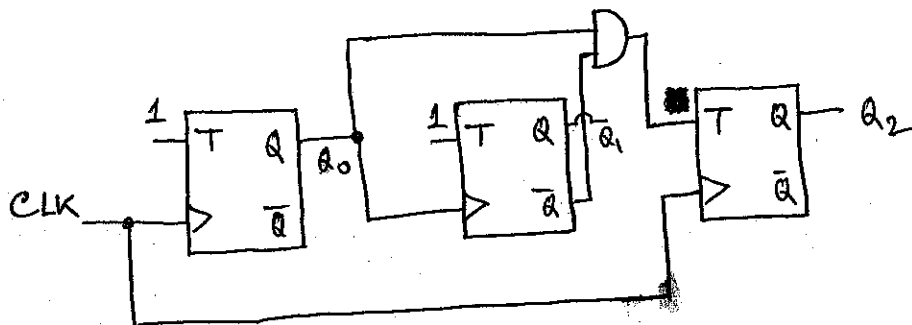


FIGURE P6(a)

 


FIGURE P6 (b)

 


FIGURE P6 (c)