

Bachelor of Engg. (Chemical Engg Examination) 2019  
Second Year, First Semester Exam., 2019  
**ELEMENTARY ELECTRONICS**

Time : Three hours

Full Marks: 100

*All parts of the same Section/question must be answered at ONE place only*

**A. Answer any two(2) questions from this Section A [among (a), (b) and (c)]**

1. (a) i. Forbidden energy gap for silicon is \_\_\_\_\_.  
 ii. Semiconductors have \_\_\_\_\_ temperature coefficient of resistance.  
 iii. The conductivity of an intrinsic semiconductor \_\_\_\_\_ with temperature.  
 iv. The mobility of charge carriers has the unit \_\_\_\_\_.  
 v. Why intrinsic semiconductors behave like an insulator at low temperatures?  
 vi. Define diffusion current and drift velocity in a semiconductor. [1+1+1+1+3+3]

- (b) i. An ideal diode offers \_\_\_\_\_ resistance when forward biased and \_\_\_\_\_ resistance when it is reverse biased.  
 ii. Draw and explain the VI characteristics of a PN junction diode. Write the volt-ampere equation for a PN diode (explain meaning of each symbol)  
 iii. What is forbidden energy gap? Explain.  
 iv. Draw the energy band diagram for a PN junction diode under open circuited condition. [2+4+2+2]

- (c) i. Describe Light-Emitting Diodes.  
 ii. Name the elements which are used as N-type impurities and P-type impurities.  
 iii. What do you mean by transition capacitance in PN-junction?  
 iv. What is meant by the term "Barrier potential"? What is the value for Germanium diode? [3+2+3+2]

**B. Answer any three(3) questions from this Section B [among (a), (b), (c) and (d)]**

2. (a) i. Draw the circuit diagram of bridge rectifier and explain its operation.  
 ii. Discuss the working of full-wave rectifier circuit with shunt capacitor filter, give the output voltage waveform.  
 iii. Define clamper. [4+4+2]

- (b) i. An n-channel depletion type MOSFET is operated in the pinch off region. If  $I_{DSS}=15\text{mA}$  and  $V_P=-4\text{V}$ , calculate  $I_D$  when :  $V_{GS}=-3\text{V}$  and  $V_{GS}=+2.5\text{V}$ .  
 ii. Compare depletion type MOSFET and enhancement type MOSFET  
 iii. Draw and explain different operating regions in the drain characteristics of depletion type MOSFET. [4+2+4]

- (c) i. Draw an emitter bias circuit and obtain the value of d.c. voltage and currents in the circuit.  
 ii. For a fixed bias circuit using silicon npn transistor, the value of  $\beta$  is 100. If  $V_{CC}=6\text{V}$ ,  $R_C=2\text{K}\Omega$  and  $R_B=530\text{K}\Omega$  then determine its operating point.  
 iii. Define stability factor.

- (d) i. State whether the statement is true or false: [4+4+2]  
 i.i In P-type semiconductor, the majority carriers are hole.  
 i.ii A full-wave rectifier utilizes only positive half cycle.  
 i.iii For a half-wave rectifier :  $\text{PIV} = 2V_m$ .  
 i.iv A transistor can be treated as a two port network.  
 ii. Distinguish between zener breakdown and avalanche breakdown.  
 iii. What is  $I_{CBO}$  and  $I_{CEO}$ ? Define thermal runaway in BJT.. [1+1+1+1+3+3]

[ Turn over

**C. Answer any one(1) question from this Section C [either (a) OR (b)]**

3. (a) i. Define IC.  
 ii. What is differential inputs and common inputs in op-amp?  
 iii. Define slew rate.  
 iv. Draw and explain the subtractor circuit using an op-amp

[2+2+2+4]

- (c) i. Write the properties of an ideal op-amp.  
 ii. Explain virtual ground in an op-amp.  
 iii. Draw the circuit diagram of an op-amp integrator and show that output voltage is an integration of the input voltage.

[3+3+4]

**D. Answer any two(2) questions from this Section D [among (a), (b), (c) and (d)]**

4. (a) i. Convert base of the following numbers:

- i.i.  $(65.35)_{10} \equiv (?)_{16}$   
 i.iii.  $(7CA3)_{16} \equiv (?)_{10}$   
 i.iv.  $(1745.246)_8 \equiv (?)_{16}$

- ii. Obtain 2's complement of  $(111010)_2$  and  $(101011)_2$ .  
 iii. Perform Binary Subtraction (i)  $(10010)_2$  from  $(110101)_2$  (ii)  $(1001)_2$  from  $(1101)_2$

[6+2+2]

- (b) i. State De-Morgan's theorem. Show its logic implementation.  
 ii. Simplify the following Boolean expression:

$$f = (A + \overline{BC}) + (\overline{A + \overline{BC}}) \text{ and } f = AB + ABC + \overline{AB} + \overline{ABC} \quad [4+6]$$

- (c) i. Realize the Boolean expressions using basic gates  $f = (D(\overline{A + B}) + \overline{BCD})$   
 and  $f = (\overline{AB} + A + \overline{B + C})$

- ii. Add  $(48)_{10}$  and  $(27)_{10}$  and  $(83)_{10}$  and  $(54)_{10}$  using BCD numbers.  
 iv. Convert  $(1001)_2$  to gray code and  $(1100)_2$  gray code to binary code. [6+4+2]

- (d) i. Draw the symbols of universal gates. Write their truth table (for 2-input gate).  
 ii. Realize AND, OR and X-OR using only NAND gates. [4+6]

**E. Answer any one(1) question from this Section E. [either (a) or (b)]**

5. (a) i. Distinguish between combinational circuit and sequential circuits.  
 ii. What is flip-flop?  
 iii. Describe the working of SR flip-flop with circuit diagram and truth table.

[3+3+4]

- (b) i. What is the difference between latch and flip-flop?  
 ii. What is clock? What is the purpose of the clock signal?  
 iii. Draw the circuit diagram of JK flip-flop.  
 iv. What is race around in JK flip-flop?

[2+3+2+3]