

B.E. Electronics and Telecommunication Engineering
1st Year 2nd Semester Examination 2019 (old)
Circuit Theory

Time: 3 hours

Full Marks: 100

Answer all the parts of a question in the same place

All questions carry equal marks

Answer any ten questions

1. a) A $20\ \mu\text{F}$ capacitor is connected in parallel with a $40\ \mu\text{F}$ capacitor and the combination is connected across a time-varying voltage source. At a particular time, the current supplied by the source is 5A . Obtain the magnitude of currents through the individual capacitors.
- b) In an inductive circuit the applied voltage is $V_m \sin(\omega_m t)$. Obtain the expression for instantaneous power.
- c) Find the condition under which the maximum current will be obtained for the circuit shown in Fig. 1.

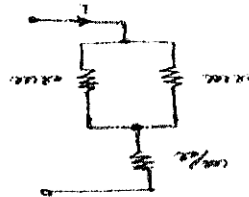


Fig-1

(3+4+3)

2. a) In the circuit shown in Fig. 2, find I and I_L .

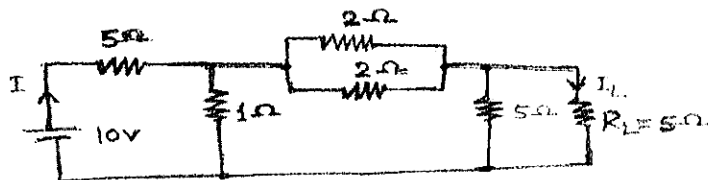



Fig 2

- b) A voltage source $v(t)$ is connected across a capacitor of 2F . Find the energy stored in the capacitor from $t=0$ to 10 sec , if $v(t) = t^2 e^{-2t}$.

(6+4)


[Turn over

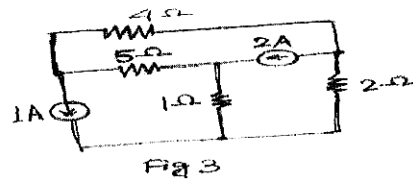3. a) State maximum power transfer theorem.
 b) In the network configuration shown in Fig. 3, find the voltage drop and current through the 5Ω resistor.




(2+8)

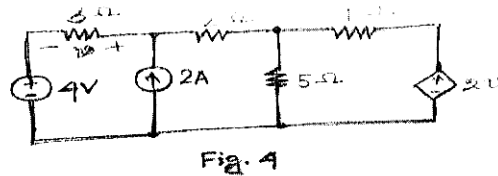4. Find v using the principle of superposition in Fig. 4.




(10)

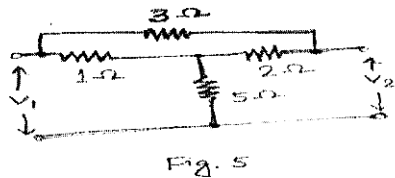5. Obtain the open circuit impedance parameters of the network shown in Fig. 5.




(10)

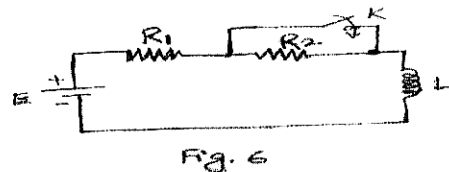6. a) Obtain the Laplace transform of $f(t) = 1 - e^{-\alpha t}$, where α is a constant.
 b) In Fig. 6, the battery voltage is applied for a steady state period. Determine the complete expression for the current after closing the switch K, where $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1\text{ H}$, and $E = 10\text{ V}$.



(3+7)

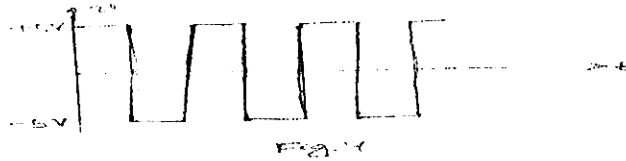7. A periodic square wave voltage as shown in Fig. 7 is applied across a 5Ω resistance. Find the expression for current using Fourier series method.



(10)

8. a) Explain under what conditions an R-C circuit behaves as an integrator and a differentiator.
 b) Calculate the series and parallel resonant frequencies of a capacitor of capacitance $0.005 \mu\text{F}$ and an inductor of inductance 100 mH and a resistance of 250Ω . Also calculate impedances at series resonance and parallel resonance.
9. a) Determine the response of a series R-C circuit for a sinusoidal input voltage.
 b) An R-L series circuit draws a current of 1 A when connected across a 10 V , 50 Hz A.C. supply. Assuming the resistance to be 5Ω , find the inductance of the circuit and power factor.
10. a) Write the expression for convolution integral and explain its application in circuit analysis.

- b) In the network shown in Fig. 8, the switch S is closed and the steady state is attained. At $t = 0$, the switch is opened. Determine the current through the inductor using Laplace transform method.

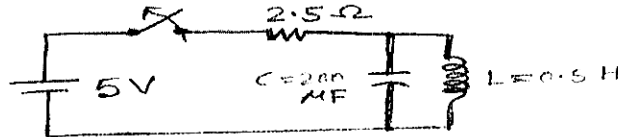


Fig. 8

(5+5)

11. a) Calculate the transient response of a series R-L circuit under a D.C. excitation voltage.
 b) In the circuit shown in Fig. 9, find $v_c(t)$ across the capacitor after switching at $t = 0$, where $R_1 = R_2 = 10 \Omega$, $R_3 = 5 \Omega$, $C = 100 \mu\text{F}$ and $V = 20 \text{ volts}$.

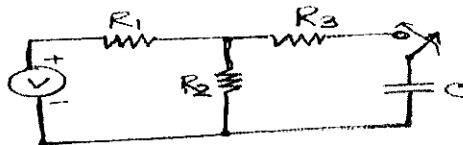


Fig. 9

(6+4)

12. a) What do you mean by incidence matrix? Write the steps to obtain reduced incidence matrix from a graph. Develop the tie-set matrix for the graph shown in Fig. 10.

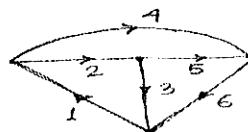


Fig. 10

(2+4+4)