

**B. E. ELECTRICAL ENGINEERING 2ND YEAR 1ST SEMESTER
SUPPLEMENTARY EXAMINATION, 2024**

Subject: CIRCUIT THEORY


Time: Three Hours

Full Marks: 100

Part I (50 marks)Use Separate Answer-script for Each PartAnswer Any Three questions (3×16)(Two marks are reserved for well-organized answers)Question
No.

Marks

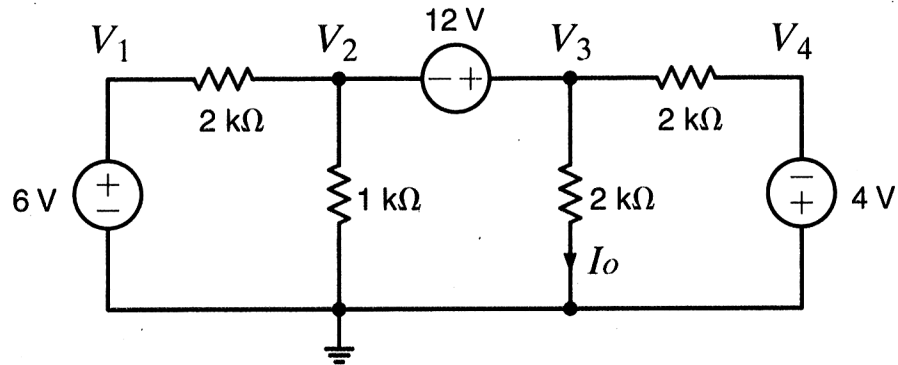
- Q1 (a) For the circuit shown in Figure Q1(a) find I_o following the concept of Super node.



8

Figure Q1(a)

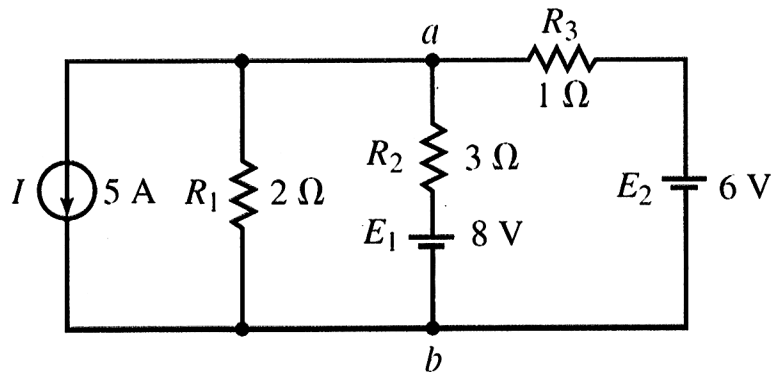
- (b) Determine the current through the 8-V battery using Mesh analysis for the circuit shown in Figure Q1(b).



8

Figure Q1(b)

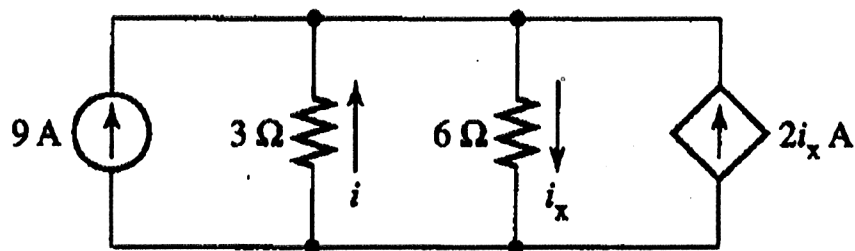- Q2 (a) Consider the circuit shown in Figure Q2(a) that contains a current-controlled-current-source. Find the value of current i .



8

Figure Q2(a)

- Q2 (b) If the indicated portion in the circuit of Figure Q2(b) is to be replaced with a current source and a 240-ohm shunt resistor, determine the magnitude and direction of the required current source.

8

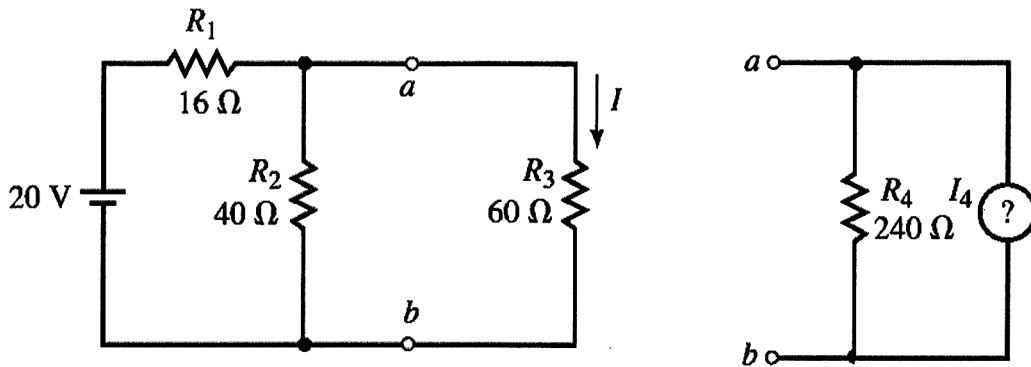


Figure Q2(b)

- Q3 (a) For the circuit shown in Figure Q3(a) obtain the Thevenin equivalent circuit across the terminal A-B.

8

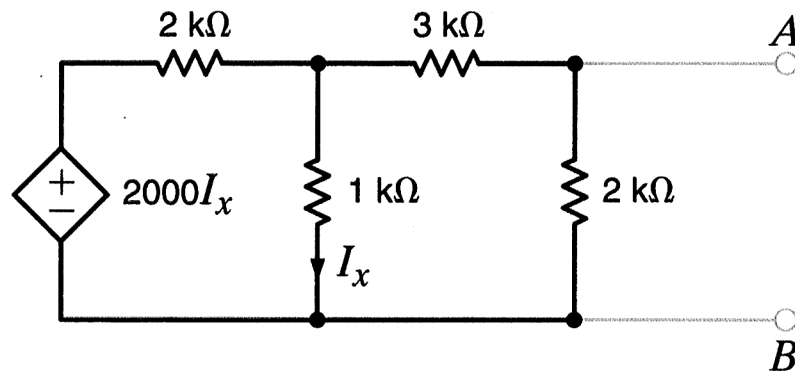


Figure Q3(a)

- (b) For the circuit shown in Figure Q3(b) determine the currents I_1 and I_2 .

8

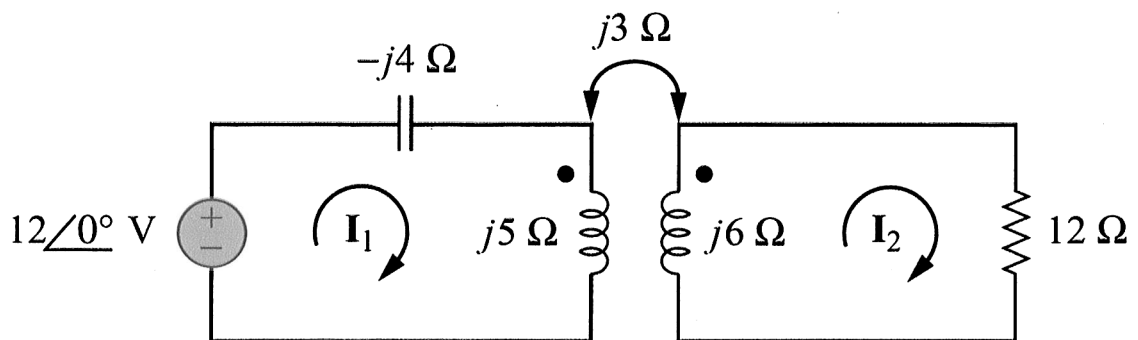


Figure Q3(b)

- Q4 (a) Find the total inductance of the series coils shown in Figure Q4(a).

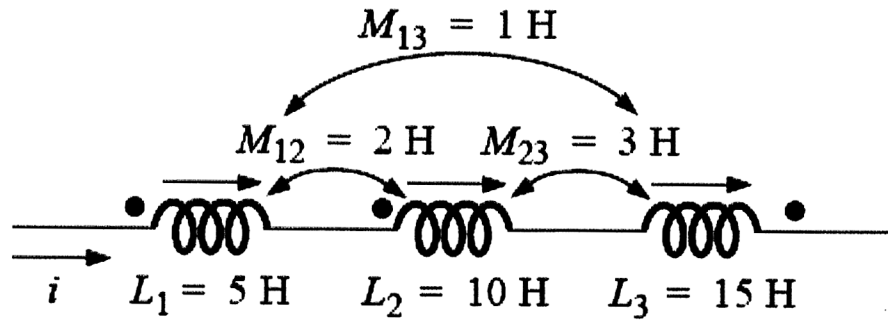


Figure Q4(a)

- (b) Draw a graph and obtain the Incidence Matrix for the network shown in Figure Q4(b).

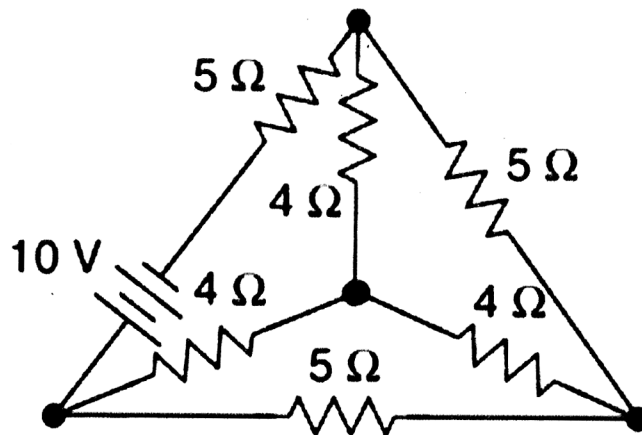


Figure Q4(b)

- (c) For the network shown in the Figure Q4(c), draw a graph of the network and obtain the fundamental Cut-Set matrix.

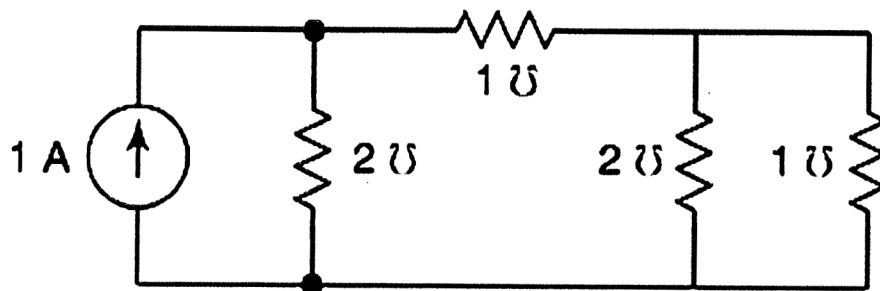


Figure Q4(c)

- Q5 (a) For the network shown in the Figure Q5(a), draw a graph of the network and prepare a Tie-Set schedule.

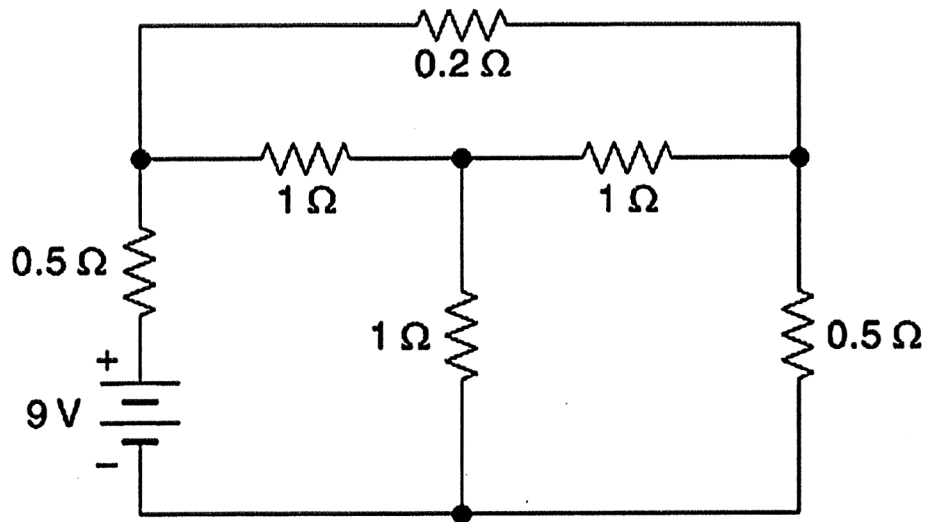


Figure Q5(a)

- (b) Assume that a steady state has been reached before the switches are operated at $t = 0$, as shown in the circuit in Figure Q5(b).

Using Laplace Transform technique obtain the expression for $V_o(s)$.

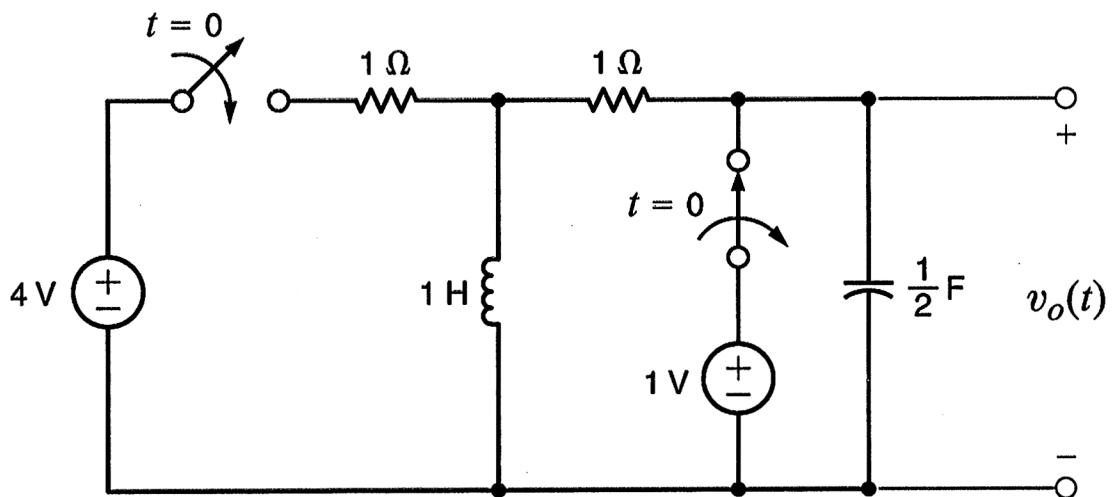


Figure Q5(b)

**B.E. ELECTRICAL ENGINEERING SECOND YEAR FIRST SEMESTER
SUPPLEMENTARY EXAM 2024
SUBJECT: - CIRCUIT THEORY**

Time: Three hours

Full Marks: 100
(50 marks for this part)

Use a separate Answer-Script for each part

No. of Question		PART -II Answer any Three (Two marks reserved for well organized answers)	Marks
1)	a)	Find the current $i(t)$ in a series RLC circuit comprising of a resistor $R = 4 \Omega$, inductor $L = 1 \text{ H}$ and capacitor $C = 1/3 \text{ F}$ when each of the following source voltage signals is applied: (i) $9r(t-2)$ (ii) $4u(t-3)$ and (iii) $2\delta(t-1)$.	(8)
	b)	Find the Laplace transform of the waveform given in Fig P-1(b). Derive the formula you used.	(8)
		Fig. P -1(b)	
2)	a)	For the circuit given in Fig.P-2(a) the circuit parameters are $R = 10\text{k}\Omega$, $L = 800 \text{ mH}$ and $C = 100\text{nF}$. The switch is closed at $t=0$. If $V_{dc} = 70 \text{ V}$, find: (i) $v_o(t)$ for $t \geq 0$ (ii) $i_o(t)$ for $t \geq 0$ (iii) Use initial and final value theorems to check the initial and final values of current and voltage.	(10)
	b)	Find the convolution of two identical rectangular pulses. Each rectangular pulse has unit amplitude and duration equal to $2T$ seconds. Also, the pulse is centered at $t=T$.	(6)
			(please turn over)

| Turn over

**B.E. ELECTRICAL ENGINEERING SECOND YEAR FIRST SEMESTER
SUPPLEMENTARY EXAM 2024
SUBJECT: - CIRCUIT THEORY**

Time: Three hours

Full Marks: 100
(50 marks for this part)

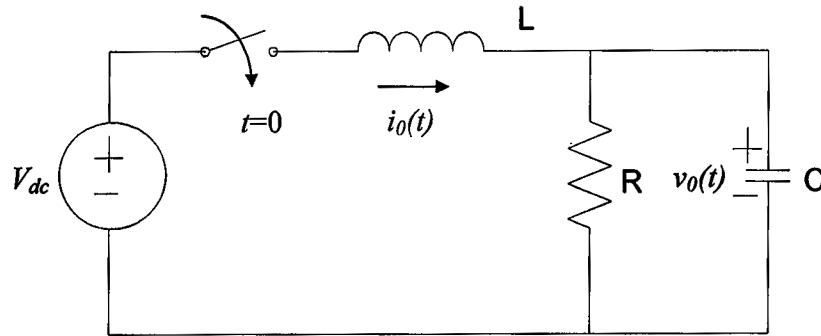


Fig. P-2(a)

- 3) a) Find the Z-parameters of the circuit given in Fig.P-3(a).

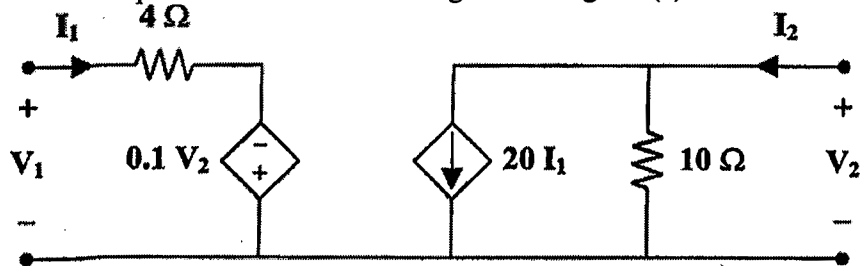


Fig. P-3(a)

- b) Determine the condition of reciprocity and symmetry in terms of ABCD parameters.

- 4) a) Determine the Y-parameter of the network given in Fig.P-4(a).

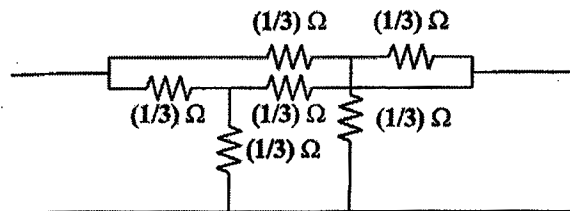


Fig. P-4(a)

(please turn over)


Ref No:

Ex/EE/PC/B/T/212/2024(S)

**B.E. ELECTRICAL ENGINEERING SECOND YEAR FIRST SEMESTER
SUPPLEMENTARY EXAM 2024
SUBJECT: - CIRCUIT THEORY**

Time: Three hours

Full Marks: 100
(50 marks for this part)

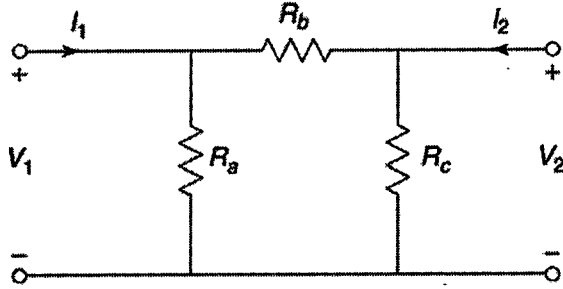b)	<p>Admittance parameters of the two port network of Fig.P-4(b) are given as: $Y_{11}=0.09$ mho, $Y_{12}=Y_{21}= -0.05$ mho, and $Y_{22}=0.07$ mho. Determine the values of R_a, R_b, R_c.</p>  <p align="center">Fig. P-4(b)</p>	(8)
5)	<p>Write short note on: (any two)</p> <p>(a) Significance to Two-Port Network Model in Electrical Engineering</p> <p>(b) H-parameter representation of BJT and the advantage gained thereof.</p> <p>(c) Complex frequency.</p>	(8+8)