

B. E. ELECTRICAL ENGINEERING 2ND YEAR 2ND SEMESTER EXAMINATION, 2024**Subject: SEQUENTIAL SYSTEMS & MICROPROCESSOR Time: 3 Hours Full Marks: 100****(50 Marks for each Part)****Use a separate Answer-script for each Part****Part I** (50 marks)

Question

Question 1 is compulsory


Marks

No.

Answer Any Two questions from the rest (2×20)Q1 Answer **any Two** of the following:

- (a) Explain the PRESET and CLEAR operations with respect to D Flip-Flop. 5
- (b) A fictitious flip-flop with two inputs A and B such that for AB= 00 and 11 the output becomes 0 and 1, respectively. For AB= 01, flip-flop retains previous output while output complements for AB= 10. Draw the truth table and excitation table of this flip-flop. 5
- (c) Starting from the excitation table develop the state diagram for J-K flip-flop. 5
- (d) What are Synchronous and Asynchronous Counters? What are the basic differences between them? 5

- Q2 (a) What is Excitation Table for a Flip-flop? With the help of Excitation Table show how SR-flip-flop can be converted to JK-flip-flop. 2+6
- (b) (i) With the help of timing diagram show that the circuit shown in Figure Q2(b) is a Mod-3 counter.
- (ii) If one connects the B output of the counter to the clock input of another J-K Flip-Flop, with both J and K of the 3rd Flip-Flop connected to +V_{CC}, draw the waveforms for the three JK flip-flop outputs.

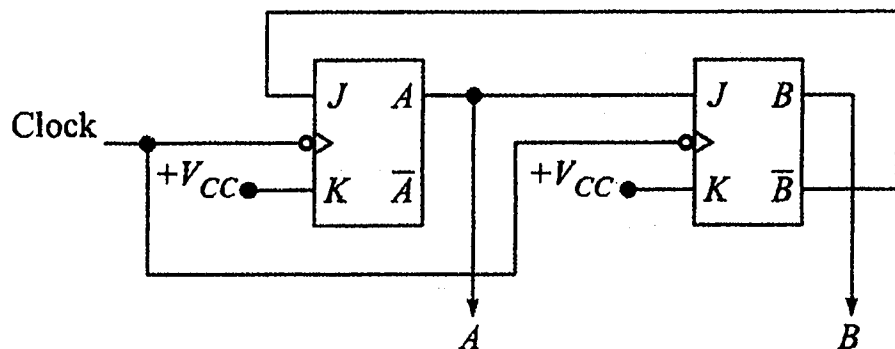**Figure Q2(b)**

6+6

[Turn over

- Q3 (a) Draw the block diagram of a 4-bit Shift-Right Register realized using D flip-flops. Show, with the help of timing diagram, how “0100” can be entered serially into the register. 4+8
- (b) Design a modulo-4 irregular counter with the counting sequence as shown in Figure Q3(b) using D flip-flop.

 


Figure Q3(b)

- Q4 (a) With the help of a schematic diagrams explain the basic difference between the Mealy and Moore models of Finite State Machine. 6
- (b) Consider the timing diagram, as given by Figure Q4(b), for a synchronous sequential logic circuit that has two inputs X and Y and one output Z . Derive (i) the State Diagram and (ii) the State Synthesis Table for a Mealy Model of the circuit and (iii) realize the circuit with the help of D flip-flops.

 


Figure Q4(b)

- Q5 (a) What is Universal Shift-Register? With the help of a neat diagram briefly explain the different modes of operation for 4-bit Universal Shift-Register. 2+8
- (b) Suppose we wish to design a circuit that detects a sequence of three or more consecutive 1s in a string of bits coming through an input line (i.e., the input is a serial bit stream).
- (i) Draw the corresponding state transition diagram. 4+6
- (ii) Obtain, with the help of state table, the logic circuit for the sequence detector realized employing D flip-flops.

B.E. ELECTRICAL ENGINEERING SECOND YEAR SECOND SEMESTER EXAM 2024

SEQUENTIAL SYSTEM AND MICROPROCESSORS

Time: Three hours

(50 marks for each Part)

Full Marks: 100

Use a separate Answer-Script for each Part

PART- II

Group-A

Answer any four questions:

4X5=20

- 1) Explain with suitable diagram why de-multiplexing of address and data bus is required?
- 2) Distinguish the operation between program counter and stack pointer 16-bit registers
- 3) What do you mean by wait state? Explain the operation of wait state generator showing typical circuit.
- 4) Explain why image address for memory address decoding will form. How this problem can be eliminated? Giving example.
- 5) Define instruction cycle, machine cycle and T-state.
- 6) Distinguish between memory mapped I/O and I/O mapped I/O address decoding method with necessary example.
- 7) Distinguish between the operation of interrupt service routine (ISR) and subroutine. Give example.
- 8) Explain how RIM instruction is used to sense the pending interrupts with the help of word format.

Group-B

Answer any three questions:

3X5=15

- 1) Draw the timing diagram of a memory read bus cycle. Suppose the READY signal becomes low at the middle of second T state. Draw the timing diagram for the modified memory read bus cycle.
- 2) Show the timing diagram for STA <16-bit operand> which consumes 3 machine cycles and 10 T states. The hex code for STA is 32H.
- 3) What are vectored interrupts? How is the address of the Interrupt Service routine calculated in vectored interrupts? Explain with an example.

[Turn over

- 4) The 8085 CPU is operated with clock frequency 3.77 MHz. Find out the time delay in sec can be produced by following programme:
- ```

 LXI B, 0FFFFH; 10 T-states
BACK: DCX B ; 6 T-states
 MOV A, C ; 4 T-states
 ORA B ; 4 T-states
 JNZ BACK ; 10 T-states

```
- 5) Draw diagram for interfacing RAM of size 2K and I/O with 8085 CPU at address 2000H and 4000H for RAM and 17H and 07H for I/O. Use partial memory and I/O address decoding method.
- 6) Discuss the control word format of 8255 PPI interfaced with 8085 CPU in BSR mode with suitable example.
- 7) What is meant the priority of interrupt system? How vector interrupt in 8085 CPU is masked?

#### Group-C

Answer any three questions:

3X5=15

- 1) Write an assembly language programme to form two arrays, one which will store even no and the other which will store odd no from a given arrays N numbers.
- 2) Write an assembly language programme to sort a given array of N elements in ascending order. Also find the count for repeated no. in the unsorted array.
- 3) Write 8085 Assembly language program to find the factorial of an 8-bit number. Draw the flow chart of the algorithm used.
- 4) Write an assembly language program in 8085 microprocessor to find square root of a number.
- 5) Write an assembly language programme to convert 2-digit BCD number into 8-bit binary number. Draw the flow chart of the algorithm used.
- 6) Write an assembly language programme to generate a pulse of duration 1 ms via I/O port with address 01H. The pulse must be initiated by pressing a push button connected to RST 7.5 vector interrupt pin of 8085 CPU.