B.E. ELECTRICAL ENGINEERING SECOND YEAR SECOND SEMESTER - 2024 ELECTRICAL MACHINES-II

Time: Three hours

Full Marks: 100

(50 marks for each part)
(Use separate Answer Script for each part)

PART - I

1. Answer any four from the following:

4x2.5

- (a) Why an induction machine is called a generalized transformer?
- (b) What will be the direction of rotation of the rotor, if the primary winding is placed on the rotor of a poly-phase induction motor?
- (c) What is the relative speed between the magnetic field produced by stator winding and the magnetic field produced by the rotor winding? Give reasons for your answer.
- (d) Find an expression for peach factor for a short peached winding.
- (e) What is deep bar rotor induction motor? How it produces high starting torque?
- 2. Answer any one from (a) and (b):

10

- (a) Explain how a rotating magnetic field with constant amplitude is generated in an three phase induction machine.
- (a) Derive an expression for developed torque of an induction motor. Also derive the value of slip for which torque is maximum and draw the torque-speed characteristics.
- 3. Answer any one from (a) and (b):

10

- (a) From the basic principle develop the equivalent circuit of a poly phase induction motor.
- (b) How can you determine the equivalent circuit parameters in the laboratory?
- 4. Answer any one from (a) and (b):

10

(a) i) If the stator impedance of an induction motor is neglected show that:

$$T_e/T_{em} = 2/(s_{mT}/s + s/s_{mT})$$

- ii) From the equivalent circuit of a poly phase induction motor, obtain the following relations:
 - 1) $I_{2st} / I_2 = \sqrt{[(s^2 + s_{mT}^2)/(s^2(1 + s_{mT}^2))]}$
 - 2) $I_{2mT} / I_2 = \sqrt{[0.5 (1 + (s_{mT}/s)^2)]}$

Ex/EE/PC/B/T/222/2024

- (b) Describe a double cage induction motor. Draw and explain the equivalent circuit of double cage rotor induction motor.
- 5. Answer any one from (a) and (b):

10

- (a) The rotor resistance and standstill reactance of a 3-phase induction motor are 0.012 ohm and 0.08 ohm per phase respectively. The full load slip is 4% at normal voltage. Calculate the percentage reduction in stator voltage to develop the full-load torque at 75% of full-load speed.
- (b) The standstill impedances of the two cages of a double-cage induction motor are (3.2 + j 1.2) ohm and (0.5 + j 6.5) ohm respectively. If the full-load slip is 5%, then find the ratio of starting torque to full-load torque. Neglect magnetizing current and stator impedance.

Ref No. : Ex/EE/PC/B/T/222/2024

Bachelor of Electrical Engineering, 2nd Year 2nd Semester Examination, 2024

SUBJECT: ELECTRICAL MACHINES-II

Time: Three Hours

Full Marks: 100 (50 each part)

Use a separate Answer-Script for each part PART - II

Answer any three questions. Question no. 3 carries 18 marks.

1. Correct and/or justify following.

4x4=16

- (i) Delta-star is more preferable than star-star without neutral three phase transformer.
- (ii) The cross section of the central limb of a shell type transformer is usually designed to have larger cross section to avoid flux saturation.
- (iii) The 9nth harmonics of magnetic flux are always in phase though its 7nth harmonics have a reversed phase sequence compared to fundamental.
- (iv) Vector group formation is unavoidable with 30 phase shift in case of Delta-star or Star-delta transformer.
- 2. (i) How core construction helps in reducing harmonics in a three phase 4+9+3=16 transformer?
 - (ii) Draw the connection diagram and phasor diagram of the following connections.
 - a) Dy1, b) Yz1 and c) Yd1
- (iii) Yy0 and Dd6 connected transformers cannot be connected in parallel-explain
- 3. (i) Show that by using two single phase transformers with proper taps, 7+11=18 three phase power supply is possible from a two phase supply.

PART - II

- (ii) In Scott-connected transformers, teaser transformer supplies 0.75 leading power factor load of 25 kW at 220 V and main transformer supplies 0.75 power factor lagging load of 45 kW at 220 V, from a three phase input line voltage of 3300V. Determine the input 3-phase line currents. Neglect magnetizing currents and the leakage impedance drops. Draw input current phasors computed for above along with a Scott-connection diagram.
- **4. i)** Draw and explain two resistor type on-load tap changer schemes.

7+5+4=16

- **ii)** Write the advantages and disadvantages of using off-load and on-load type tap-changers.
- **iii)** Why high voltage winding of a transformer is preferred for tappings of tap-changer?
- 5. Write Short notes on:

 $8 \times 2 = 16$

- (i) Development of voltage stress along the winding of a three phase transformer for input impulse and RMS voltage. And also write the measure to be taken to withstand it.
- (ii) Tertiary windings and its applications.