

**BACHELOR OF ENGINEERING (ELECTRICAL ENGINEERING) FIRST YEAR
FIRST SEMESTER - 2024**

SUBJECT: CIRCUIT THEORY

Time: Three Hours

Full Marks: 100
(50 Marks for each part)

Use a separate Answer-Script for each part
Two marks for neat and well-organized answers

Question No.	Part-I	Marks
--------------	--------	-------

Answer any three questions

1. (a) Define a unit step function and unit ramp function. What is the relationship between the two singularity functions? 8
- (b) "The inductor can be represented as an open circuit at $t = 0+$ & The capacitor can be represented as a short circuit at $t = 0+$ " – Explain. 8
2. (a) The voltage across the capacitor in the Fig. 1 is given as follows: $v_c(t) = 2r(t) - 2r(t-1)$. Find the value of the voltage source V_s in terms of singularity functions and sketch it. 8

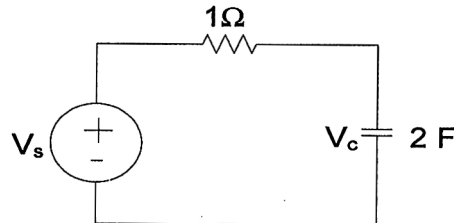


Fig. 1

- (b) Derive and draw the equivalent circuit of the Laplace transformation of inductance and capacitance with initial conditions. 8
3. (a) For the circuit shown in Fig.2, steady state is reached with the switch closed. At $t=0$, the switch is opened. In this condition, find $i_1(0+)$, $i_2(0+)$, $i_1'(0+)$ and $i_2'(0+)$. 8

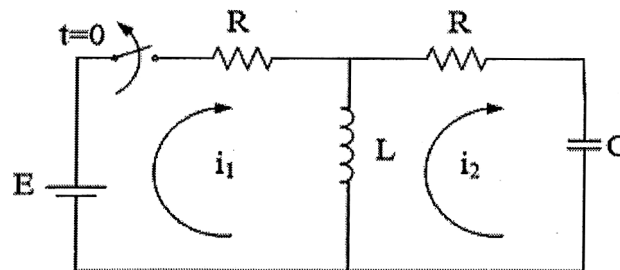


Fig. 2

- (b) State and derive the initial value theorem. Find the initial and final values of the following function using initial and final value theorem, respectively. 8

$$F(s) = \frac{s-1}{(s-2)(s+4)}$$

4. (a) Find the Laplace transform of the following three signals as shown in Fig. 3: 3×4

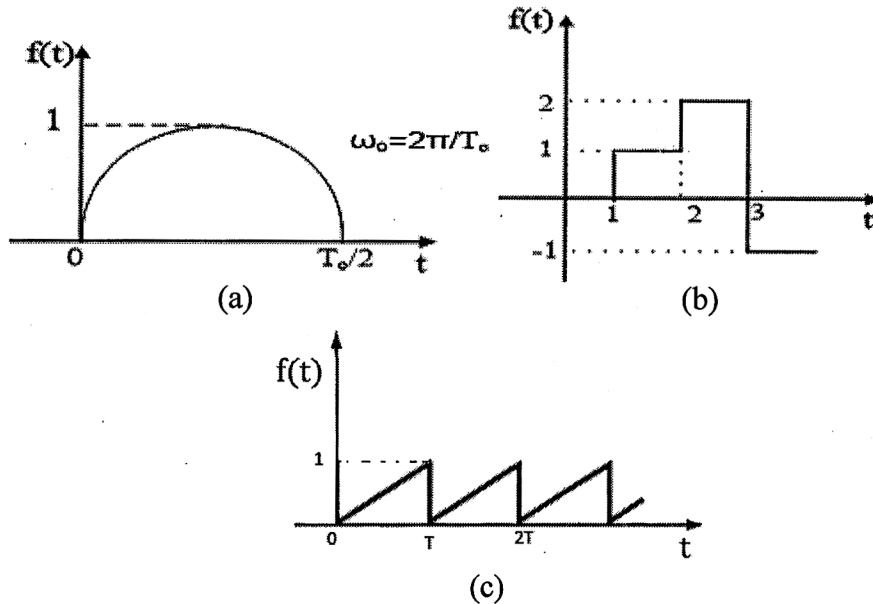


Fig. 3

- (b) What do you understand by the terms 'terminals' and 'port' in connection to networks? 4
5. (a) Draw a two port network whose ABCD parameters are $A=2, B=1 \text{ ohm}, C=1 \text{ mho}, D=2$. If two such networks are cascaded, determine the ABCD parameter of the overall network. 7
- (b) Obtain the ABCD parameters in terms of Z parameters of a two-port network. 9

BACHELOR OF ENGINEERING (ELECTRICAL ENGINEERING)

1ST YEAR 1ST SEMESTER EXAMINATION, 2024

Subject: CIRCUIT THEORY

Time: Three Hours

Full Marks: 100

Part II (50 marks)

Question

Question 1 is compulsory

No.

Answer Any Two questions from the rest (2×20)

Marks

Q1 Answer **Any One** : (a) or (b)

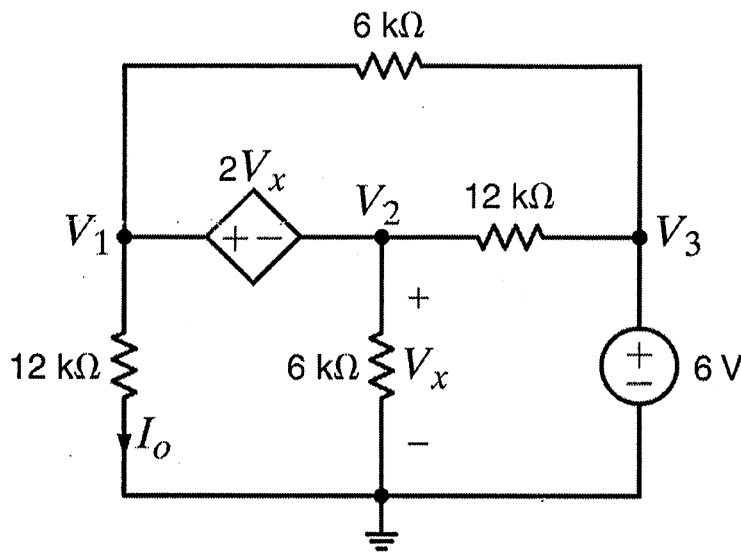


Figure Q1

(a) Determine the value of the current I_o using Loop Analysis technique.

10

OR

(b) Determine the value of the current I_o using Nodal Analysis technique.

10

Q2 (a) For the circuit shown in Figure Q2(a) to find I_o .

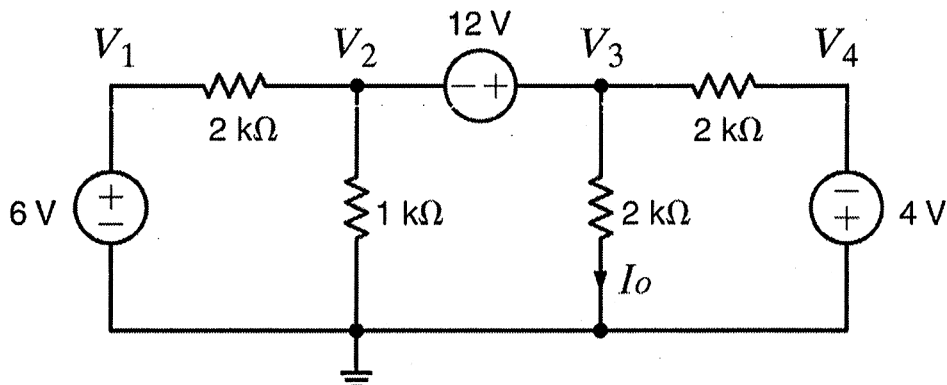


Figure Q2(a)

(b) State and prove Maximum Power Transfer Theorem.

4

- Q2 (c) For the circuit, as shown in Figure Q2(c), find the value of R that results in maximum power absorbed by R for (i) $\beta = 0.5$ and (ii) $\beta = 1.5$.

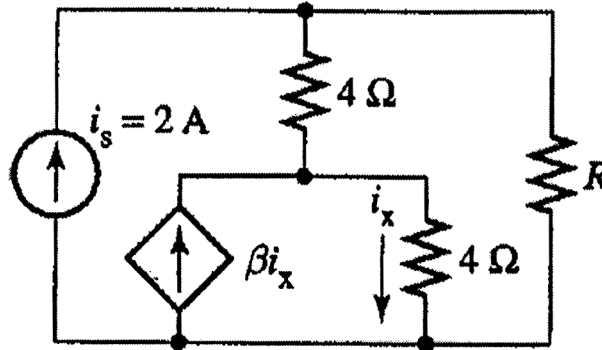


Figure Q2(c)

- Q3 (a) Find, using source superposition, the value of V_o for the circuit shown in Figure Q3(a).

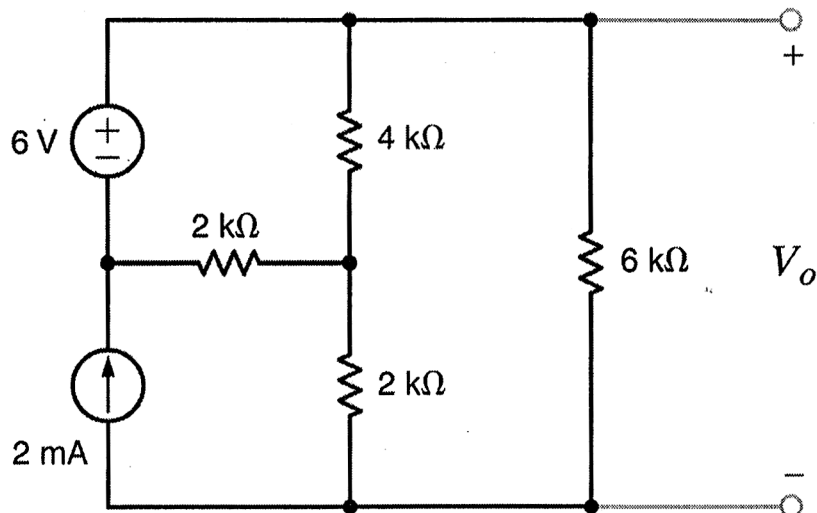


Figure Q3(a)

- (b) Two mutually coupled inductors are connected across a voltage source, as shown in Figure Q3(b). Obtain the equivalent inductance of the circuit.

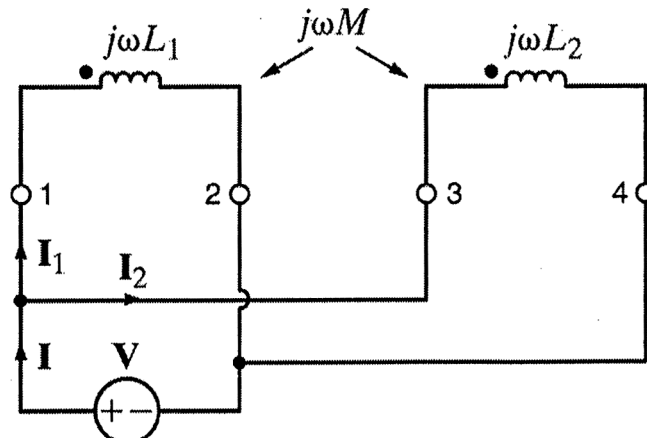


Figure Q3(b)

- Q3 (c) Calculate the mesh currents I_1 and I_2 in the circuit shown in Figure Q3(c).

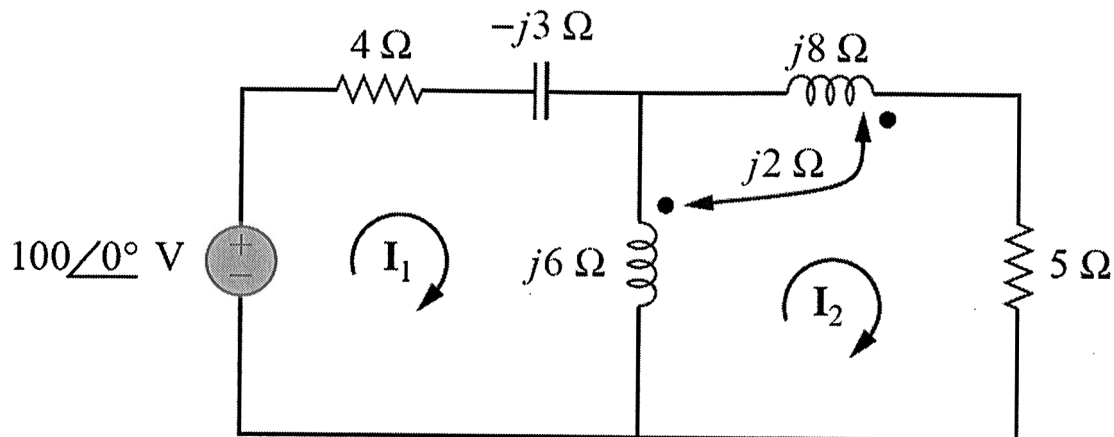


Figure Q3(c)

- Q4 (a) Consider the circuit shown in Figure Q4(a) that contains a current-controlled-current-source. Find the value of current i .

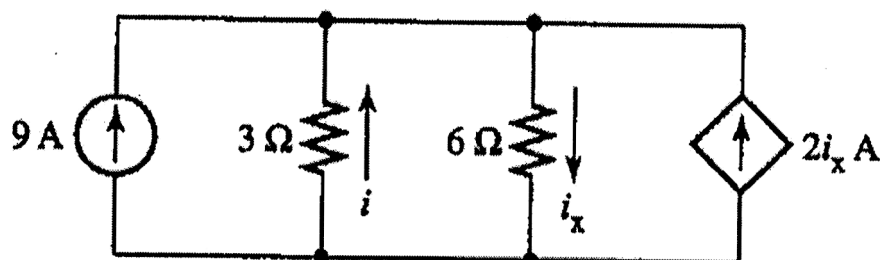


Figure Q4(a)

- (b) Draw the graph and obtain the Incidence Matrix for the network shown in Figure Q4(b).

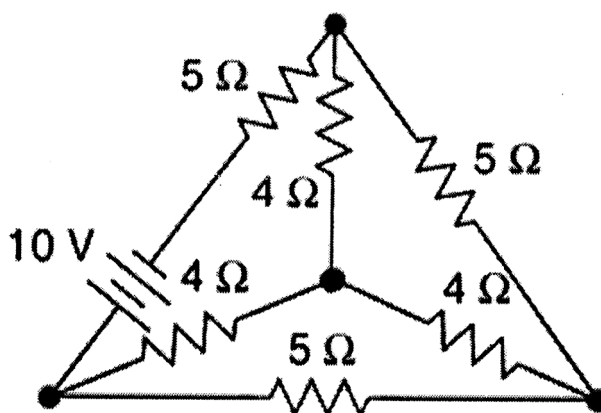


Figure Q4(b)

- (c) Define Cut-set for a network graph.

With the help of an example, show how Kirchhoff's Current Law can be written in terms of basic Cut-Set matrix.

- Q5 (a) Assume that a steady state has been reached before the switch is operated at $t=0$, as shown in the circuit in Figure Q5(a). Using Laplace Transform technique obtain the expression for $V_o(s)$.

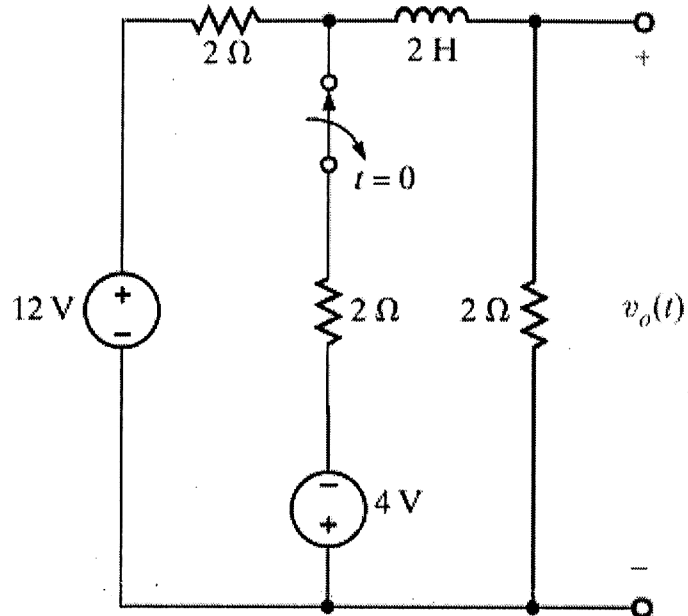


Figure Q5(a)

- (b) For the network shown in the Figure Q5(b), draw the oriented graph and obtain the Tie-Set Matrix.

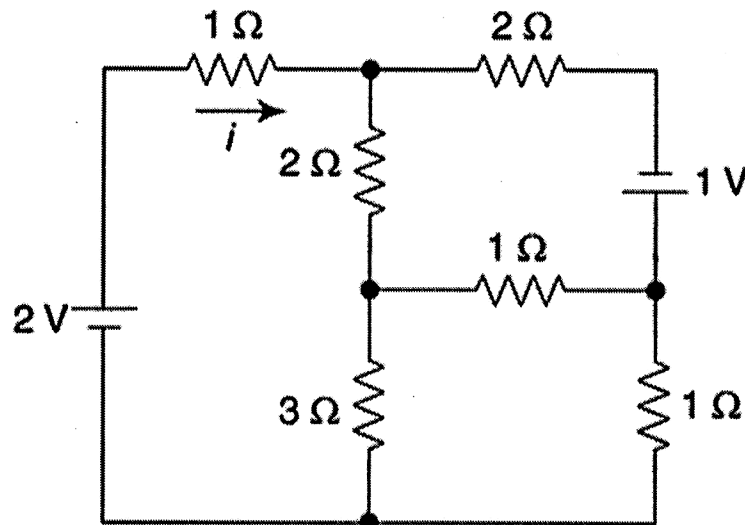


Figure Q5(b)

- (c) Find the total inductance of the series coils shown in Figure Q5(c).

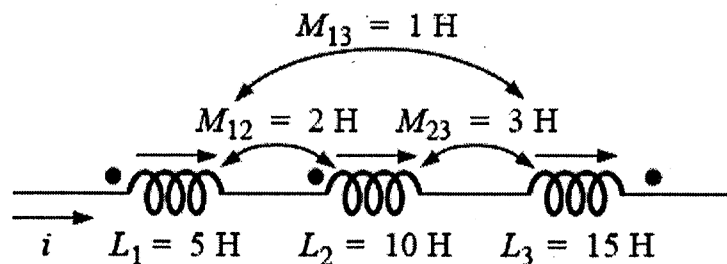


Figure Q5(c)