

EX/EE/5/T/111/2024

BACHELOR OF ENGINEERING (ELECTRICAL ENGINEERING) FIRST YEAR FIRST
SEMESTER EXAM, 2024

PRINCIPLES OF ELECTRICAL ENGINEERING - I

Time: Three hours

Full Marks 100
(50 marks for each part)

Use a separate Answer-Script for each part

	PART I Answer any three questions. Two marks are reserved for neat and well organized answers.	Marks
1.a)	Deduce the capacitance per unit length between two co-axial cylinders with the assumption that +Q Coulomb of charge is on the outer surface of the inner cylinder and the outer cylinder is earthed.	6
1.b)	Derive an expression for potential energy in an electric field.	5
1.c)	It is required to hold four equal point charges +Q in equilibrium at the corners of a square of 2 m side. Find the point charge that will do this if placed at the centre of the square. The square is placed in air.	5
2.a)	State and prove Gauss's law.	5
2.b)	Deduce an expression for force of attraction between two oppositely charged plates.	5
2.c)	An air capacitor consisting of 2 parallel plates of 50-cm side is charged to p.d. of 250 V when the plates are 1 mm apart. Find the work done in separating the plates from 1 to 3 mm. Assume perfect insulation.	6
3.a)	State and explain Biot Savart's law.	3
3.b)	Deduce expressions for the magnetic field intensity and magnetic flux density on the axis of a square coil and hence show that the magnetic field intensity at the centre of a square coil is $\sqrt{2}I/\pi a$, where 'I' is the current flowing through the coil and 'a' is half the length of any side of the square coil.	8

[Turn over

3.c)	The magnetic field due to a current carrying circular loop of radius 12 cm at its centre is 0.5×10^{-4} T. Find the magnetic field due to this loop at a point on the axis at a distance of 5 cm from the centre.	5
4.a)	Deduce an expression for magnetic field strength at a point due to a finite length of wire carrying current.	5
4.b)	Deduce an expression for the coefficient of coupling for two magnetically coupled coils.	5
4.c)	Two coils, X of 12000 turns and Y of 15000 turns, lie in parallel planes so that 45% of the flux produced by coil X links coil Y. A current of 5 A in X produces 0.05 mWb while the same current in Y produces 0.075 mWb. Calculate (a) the mutual inductance, and (b) the coupling coefficient.	6
5.a)	Derive an expression for the energy stored in a magnetic field.	4
5.b)	Deduce an expression for the eddy current loss occurring in a magnetic material.	6
5.c)	Two coils, with terminals AB and CD respectively, are inductively coupled. The inductance measured between terminals AB is $380 \mu\text{H}$ and that between terminals CD is $640 \mu\text{H}$. With B joined to C, the inductance measured between terminals AD is $1600 \mu\text{H}$. Calculate: (a) the mutual inductance of the coils; and (b) the inductance between terminals AC when B is connected to D.	6

BACHELOR OF ENGINEERING (ELECTRICAL ENGINEERING)
1ST YEAR 1ST SEMESTER EXAMINATION 2024
PRINCIPLES OF ELECTRICAL ENGINEERING-I

Time: 3 hours


Use Separate Answer script for each part

Full Marks:100

Part-II (50 Marks)**ANSWER ANY THREE QUESTIONS****QUESTION NO.1 CARRIES 18 MARKS**

Q.1. (A) State the Maximum power transfer theorem applicable for both the AC and DC circuits.

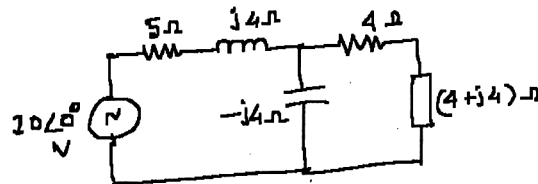(B) Apply the Thevenin's theorem to determine the value of current through 4Ω resistor-



6+12=18

Q.2. (A) A coil of resistance 50Ω and inductance 0.25H is in parallel with a circuit having 55Ω resistor and $100\mu\text{F}$ capacitor. The parallel circuit is connected to a 230V , 50Hz supply.

Calculate (i) the supply current; (ii) the equivalent circuit impedance, resistance and reactance.

(B) A voltage, given by

$$v(t) = 50 \sin \omega t + 15 \sin(3\omega t + \pi/5)$$

is applied to a circuit containing a resistance of 20Ω in series with an inductor of 0.05H with negligible resistance. If the fundamental frequency is 50Hz , calculate (i) the power dissipated (ii) the power factor for the circuit.

8+8=16

Q.3. (A) State and explain the Superposition theorem applicable for an electrical circuit.

(B) State and prove the Millman's theorem for number of voltage sources connected in parallel.

6+10=16

Q.4. (A) A $5\mu\text{F}$ capacitor, initially charged to 230V , is discharged through a $200\text{k}\Omega$ resistor. What is the capacitor voltage at 0.20s after the capacitor starts to discharge?

(B) Show that the energy $W_L(t)$ stored in an inductor 'L' is expressed by -

$$W_L = \frac{L}{2} [i_L^2(t_1) - i_L^2(t_0)]$$

where $i_L(t_1)$ and $i_L(t_0)$ are the current through 'L' at time $t=t_1$ and $t=t_0$.

6+10=16

Q.5. (A) Write down the conversion formulae of Delta-Wye and Wye-Delta network with suitable diagram.

(B) Show that required kVAR for improvement of power factor angle from Φ_i to Φ_f -

$$\text{kW} [\tan \Phi_i - \tan \Phi_f]$$

8+8=16