

B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR
FIRST SEMESTER EXAM, 2024

ANALOG CIRCUITS-I


Time: Three hours

Full Marks: 100

(All parts of the same question must be answered together)

Module I [Answer any one (1×15=15)]

 1. i. If a sine wave with $V_{pp}=5V$ applied to the input of a half wave rectifier circuit
- Sketch the input and output voltage waveforms in the same scale. [2]
 - Determine the conduction angle and the output DC voltage. Assume diode drop $=0.5V$. [4+4]
 - Calculate the % load regulation. Given that the maximum load $R_L=500\Omega$ and dynamic resistance of the diode is 50Ω . [2]
 - Find the expression for DC voltage for a half wave rectifier with a capacitor filter. [3]
- ii. a) Classify clipper circuits and explain the circuit to obtain the following output. [2+4]



- Draw and explain a negative clamper circuit. [6]
- Draw a circuit to obtain an output of $4V_p$ where V_p is the peak value of the input. [3]

Module II [Answer any one (1×10=10)]

2. i. A step input of 5V is applied to a low pass RC filter.
- Sketch the output waveform. [2]
 - Determine the expression for rise time. [4]
 - Calculate the output voltage at $t=2ms$ and $t=5ms$. The resistor R is $10k\Omega$, and the capacitor C is $100nF$. [4]
- ii. Draw a compensated attenuator circuit and explain perfect compensation, under compensation and over compensation conditions. [10]

[Turn over

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR
FIRST SEMESTER EXAM, 2024**

ANALOG CIRCUITS- I

Time: Three hours

Full Marks: 100

Module III [Answer any five (5×7=35)]

3.
 - i. Explain the origin of instability of the operating point of a BJT amplifier. Define thermal stability factors associated with BJT biasing circuits. [5×7]
 - ii. Determine the voltage gain of a CE amplifier with partially bypassed emitter resistance (draw). Given that $V_{CC}=15V$, $R_1=36k\Omega$, $R_2=15k\Omega$, $R_C=3.6k\Omega$, $R_{E1}=27k\Omega$ and $R_{E2}=1.5k\Omega$.
 - iii. Draw and explain the frequency response of a CE amplifier.
 - iv. Draw a Darlington pair in CC mode and derive the expression for input and output impedances.
 - v. Draw the load lines of a source bias JFET circuit for two values of R_S and explain the effect of R_S on stabilizing the operating point.
 - vi. For a CS amplifier with E-mode MOSFET, find the expression for voltage gain with the help of small signal equivalent circuit using h-parameters.
 - vii. Determine the operating point of the JFET amplifier. $R_D = 6.8k\Omega$, $R_S = 2.7k\Omega$, $R_{G1} = 9M\Omega$, $R_{G2} = 1M\Omega$, $R_L = 10k\Omega$, $V_{DD} = 24V$ and $V_{GS} = -3V$.
 - viii. Explain Miller effect in CS amplifier. Draw and explain a circuit to avoid Miller effect.

Module IV[Answer any five (5×5=25)]

4.
 - i. Write down characteristics of an ideal OP-Amp.
 - ii. Define offset voltage, bias current and CMRR of OP-Amp. [5×5]
 - iii. Determine common mode gain of differential amplifier if the collector resistances of the two amplifiers are not equal.
 - iv. Draw a Schmitt trigger circuit and explain the output.
 - v. Calculate the close loop voltage gain of non-inverting amplifier considering finite open loop gain.
 - vi. Draw and explain a subtractor using Op-Amp.
 - vii. Draw and write down advantages of Instrumentation amplifier
 - viii. Draw circuit to obtain $5xy+2$ at the output where x and y are voltages.

Module V[Answer any three (3×5=15)]

5.
 - i. Draw and explain shunt voltage regulator.
 - ii. Write down the IC name of fixed and adjustable positive, negative voltage regulators. What are the functions of three external capacitances during working of such ICs? [3×5]
 - iii. Explain Fold-back current limiting in a series voltage regulator.
 - iv. In LM317, determine the minimum and maximum regulated voltage. Given that $I_{adj}=50\mu A$, $R_1=220\Omega$ and R_2 is a $5k\Omega$ pot.
 - v. Draw and explain a buck switching voltage regulator.