

B.E.Tel.E. 2nd YEAR EXAMINATION, 2024
(2nd Semester)

TRANSMISSION LINES AND WAVEGUIDES

Time: Three hours

Full Marks 100

No. of
questions

Marks

Answer any *five* questions.Consider $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$ and $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

Values of other universal physical constants may be assumed, if necessary.

Usage of Smith Chart is permitted.

- | | | |
|-------|---|------|
| 1.(a) | Consider a lossless coaxial air line with inner conductor radius 'a' and outer conductor radius 'b'. Calculate its series inductance per unit length and shunt capacitance per unit length. | 8+8 |
| (b) | Hence show how its characteristic impedance would change if the inner conductor is made thicker without changing the external dimensions. | 4 |
| 2.(a) | Solving the Telegrapher's equation, derive an appropriate expression for the input impedance along a line. | 14 |
| (b) | What do you mean by a smooth line? Is an infinite line smooth? Justify your answer. | 6 |
| 3.(a) | A generator of 1V, 1kHz and internal resistance 50Ω supplies power to a 50 km open wire line terminated in a 230Ω resistance. The line parameters are $R=19.4 \Omega/\text{km}$, $L=0.00367 \text{ H/km}$, $G=9.8 \times 10^{-4} \text{ S/km}$ & $C=0.00835 \mu\text{F/km}$. Calculate the insertion loss in dB deriving all necessary formulae. | 16 |
| (b) | Why is it preferred to express the loss in dB? | 4 |
| 4.(a) | Obtain the T-section lumped equivalent circuit of a transmission line. | 10 |
| (b) | Describe the frequency domain reflectometry procedure to locate an underground line fault. | 10 |
| 5.(a) | An antenna, as load to a line, produces a VSWR of 2.8 with a voltage minimum at 0.12λ from the antenna terminals. Find the antenna impedance if $R_0=300 \Omega$ for the line. | 8 |
| (b) | Design an appropriately located short circuited stub for matching the antenna to the line, | 12 |
| 6.(a) | Discuss how to plot a Smith chart grid. | 12 |
| (b) | A 15m long RF cable with $R_0=300 \Omega$ is to be connected to a 3m long 150Ω line terminated by an 150Ω resistor. Find the length and characteristic impedance of a quarter wave transformer designed for the system. Also find the VSWR along all line segments involved. | 8 |
| 7.(a) | What is the cutoff frequency of a WR62 rectangular waveguide, whose inner cross sectional dimensions are $0.622" \times 0.311"$? Derive all relations you use. | 18 |
| (b) | For which microwave frequency band of operation is it suited? | 2 |
| 8. | Write short notes on any <i>two</i> of the followings | |
| (a) | Circle diagram of dissipationless lines | |
| (b) | Excitation of waveguides | |
| (c) | Distortion along a telephone cable | 10X2 |