

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING
SECOND YEAR SECOND SEMESTER EXAM, 2024**

ANALOG CIRCUITS- II

Time: 3 hours

Full Marks: 100

(All parts of the same question must be answered together)

use separate answer script for each part

PART-I

Answer Any Three (3×20=60)

1.
 - a) Draw and explain frequency response of R-C Coupled multistage amplifier. CO1 [5]
 - b) Discuss the advantages of using FETs in multistage amplifier configurations. CO1 [3]
 - c) Derive the expression for the overall voltage gain of a cascaded multistage amplifier consisting of two identical CE amplifier stages. CO2 [8]
 - d) Given the following parameters for each CE amplifier stage: $R_{in}=10\text{ k}\Omega$, $R_C=2\text{ k}\Omega$, $R_E=200\Omega$, $\beta=100$, and $r_{\pi}=1\text{ k}\Omega$, $R_S=500\Omega$, $R_L=12\text{ k}\Omega$, determine the overall voltage gain of the multistage amplifier. Assume coupling capacitors have negligible impedance at the operating frequency. CO3 [4]
2.
 - a) Write the advantages of cascode amplifier over CE/CS amplifier. CO1 [3]
 - b) Draw cascode amplifier using FET and explain that Miller effect can be reduced in cascode amplifier. CO1 [5]
 - c) Derive the expression for voltage gain of a cascode amplifier with the help of small signal analysis. CO2 [8]
 - d) Determine midband gain of a cascode amplifier using FET. Given that $V_{DD}=10\text{V}$, $g_m=5\text{mS}$ (both), $R_D=5\text{k}\Omega$, $R_S=1\text{k}\Omega$ (bypassed) and $R_L=5\text{k}\Omega$. CO3 [4]
3.
 - a) Classify power amplifiers with respect to their conduction angle and conversion efficiency. CO1 [4]
 - b) Draw and explain cross-over distortion in class B push-pull power amplifier. CO1 [4]
 - c) Derive the expression for power conversion efficiency of class B power amplifier. CO2 [8]
 - d) Determine the quiescent current (I_Q) and rms load current (I_L) in a Class AB power amplifier. Given that $\pm V_{CC}=10\text{V}$, $R_L=16\Omega$, $R_1=R_2=1\text{k}\Omega$ and $V_{BE}=0.5\text{V}$. CO3 [4]

[Turn over

4. a) Classify tuned amplifiers and define them. CO1 [3]
 b) Draw and explain the operation of single tuned amplifier. CO1 [5]
 c) Prove that Band width of n-stage single tuned amplifier is $BW_n = BW_1 \sqrt{2^n - 1}$ CO2 [8]
 d) Determine the resonant frequency of a single tuned amplifier. Given that the tank circuit consists of $L=1\text{mH}$ with coil resistance of 50Ω and $C=1\mu\text{F}$. CO3 [4]
5. a) Draw and explain a feedback amplifier using the voltage sampling-series mixing feedback topology. CO1 [3]
 b) Explain the effect of negative feedback on the input and output impedance of the amplifier. CO1 [5]
 c) Formulate the closed-loop voltage gain (A_{CL}) expression for a feedback amplifier using the voltage sampling-series mixing feedback topology. CO2 [8]
 d) Derive the expression for time period of a collector coupled astable multivibrator with the help of proper circuit diagram and waveforms. CO3 [4]
- Answer Any One (1×10=10)**
6. Design an audio amplifier (only gain stage) to deliver an average power of 0.1 W to an 8Ω speaker from a microphone that produces a 10 mV peak sinusoidal signal and has a source resistance of $1\text{ k}\Omega$. $V_{CC}=12\text{V}$, $\beta = 100$. Consider $I_{C1}=5\text{mA}$ and $I_{C2}=15\text{mA}$. CO4 [10]
7. Design a function generator that can generate sine, square and triangular wave. Choose proper components to set the time period of the signal to 1msec. CO4 [10]

PART-II

8. Answer either part (a) or part (b) (15)
- (a) Discuss on the differences between a relaxation oscillator and a sinusoidal oscillator with representative diagrams. CO1 [7+8]
 Derive the expression of the loop-gain and oscillation frequency of a Wien-Bridge Oscillator. CO2
- (b) Draw the circuit diagram of a Pierce oscillator and discuss its operation. CO1 [7+8]
 Derive the general expression of the frequency of oscillation of a Hartley oscillator with appropriate diagrams and explanations. CO2

9. Answer either part (a) or part (b) (15)


- (a) Design a scheme to convert a bistable multivibrator to an astable multivibrator CO4
(provide a supporting schematic as well).

[5+10]

Consider that the inductor in the tank circuit of a BJT based Colpitts Oscillator is replaced by a crystal having $L = 0.6 \text{ H}$, $C_s = 0.012 \text{ pF}$, $C_p = 4 \text{ pF}$. If one of the capacitors in the tank circuit be fixed at 10 pF while the other is variable in a range of 2 pF to 20 pF , find the range over which the oscillation frequency of the Colpitts Oscillator maybe tuned.

- (b) For the following circuit, find the loop gain $L(s)$, the frequency for zero loop phase, and the ratio R_2/R_1 for oscillation. CO4

[15]

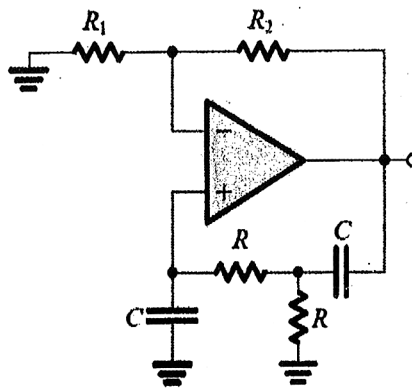

CO		CO1	CO2	CO3	CO4	Total
Marks	Part I	24	24	12	10	70
	Part II	7	8	00	15	30
	Total	31	32	12	25	100