

B. ETCE 2ND YEAR 1ST SEMESTER EXAMINATION, 2021₁
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

Answers any five questions from the followings. (5×20)

- 1) A) For the network shown in Fig.1, determine the node voltages. (10)

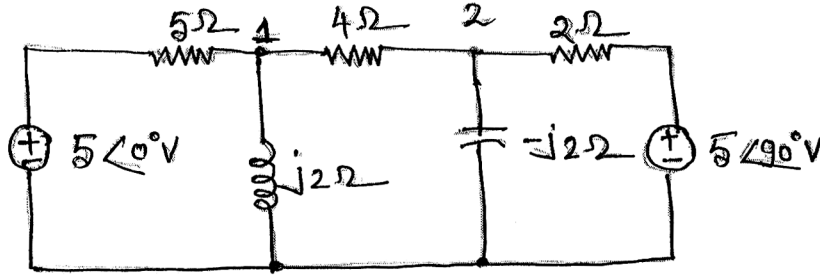


Fig. 1

- B) Determine the loop currents i_1, i_2, i_3 of the network shown in Fig.2, by mesh analysis, given $R_1=R_2=R_3=1$ ohm and $v_1=v_2=v_3=1$ volt. Assume R_4 to be negative resistance of value -5 ohms. (10)

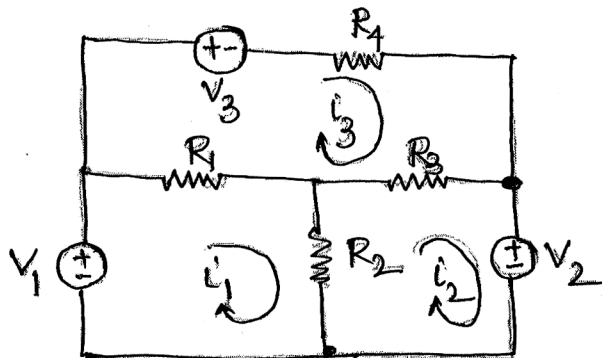


Fig. 2.

- 2) A) Determine the Fourier expansion in the exponential form for the square wave given in Fig.3. (12)

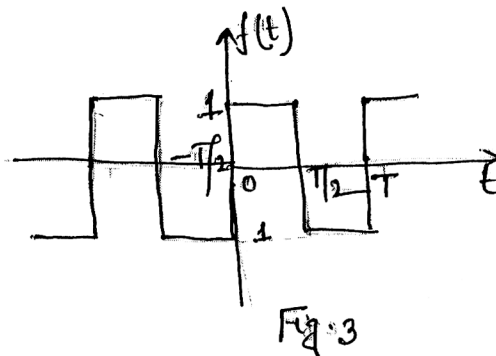


Fig. 3


[Turn over

B. ETCE 2ND YEAR 1ST SEMESTER EXAMINATION, 2021
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

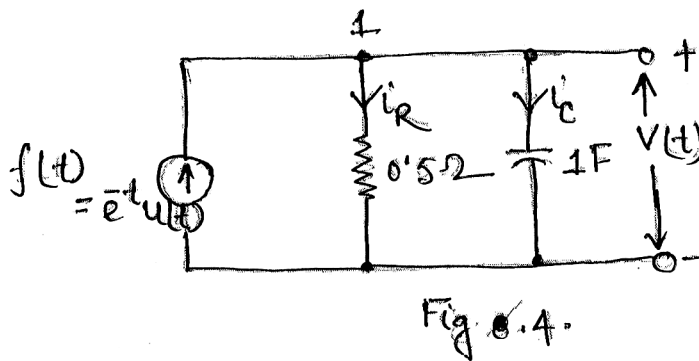B) Determine the output voltage response across the capacitor to a current source excitation $i(t) = e^{-t}U(t)$, as shown in Fig.4. (8)



3) A) Determine the Laplace transform of the following time functions

i) $t \cdot \exp(-at)$ ii) $5 \exp(-3t) \cos 5t$ (5)


B) For the given Laplace transform

$$Y(s) = \frac{17s^3 + 7s^2 + s + 6}{s^5 + 3s^4 + 5s^3 + 4s^2 + 2s}$$

Find the initial value and final value of the corresponding time function $y(t)$.

(5)

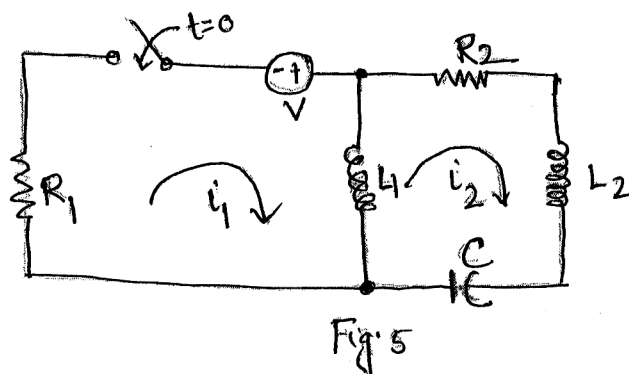C) Apply the Laplace transform method to determine the mesh current in the circuit shown in Fig.5. Assume the switch is closed at $t=0$. (10)




B. ETCE 2ND YEAR 1ST SEMESTER EXAMINATION, 2021₁
CIRCUIT ANALYSIS AND SYNTHESIS


Time: 3 Hours

Full Marks: 100

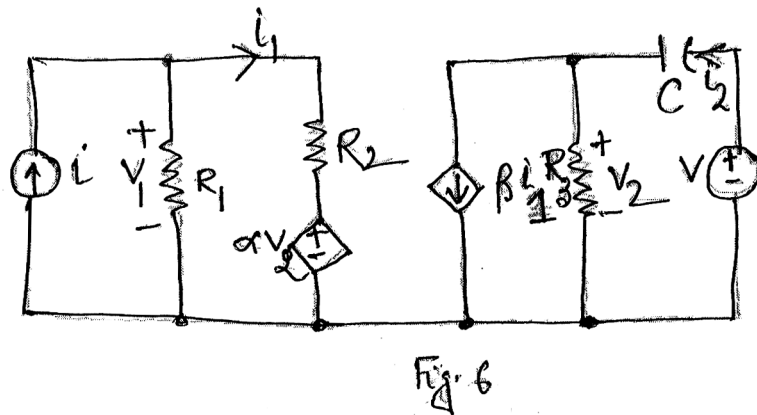- 4) A) Using the principle of superposition, calculate the voltage $V_2(t)$ in Fig.6. Assume $R_1=R_2=1\Omega$, $R_3=0.5\Omega$, $C=2F$, $\beta=2$, $\alpha=1$, $i(t)=\sin t$, $V(t)=t$. (10)



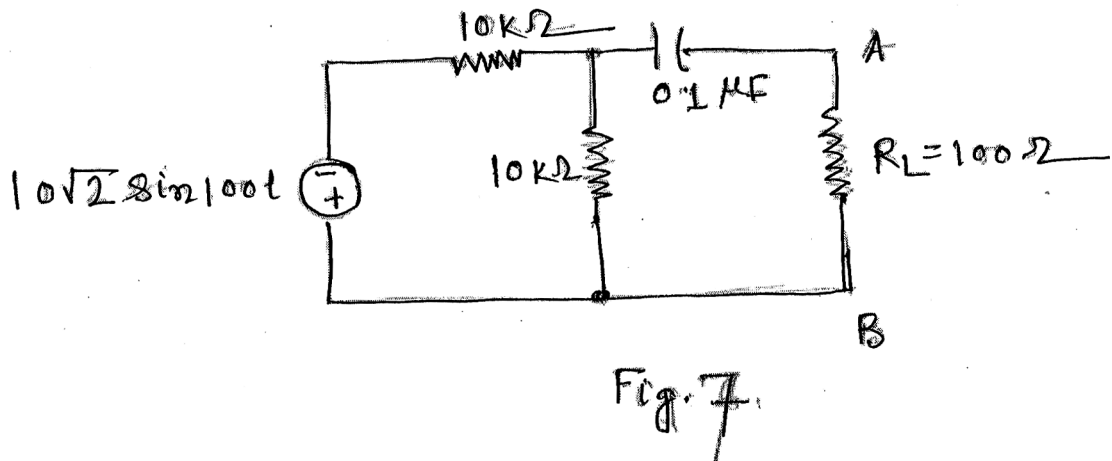- B) Find Thevenin's equivalent at terminals A,B of the network in Fig.7. Then determine the current through resistor R_L . (10)




- 5) A) An RLC series circuit has $R=1k\Omega$, $L=100mH$, $C=10\mu F$. If a voltage of 100 is applied across the series combination, determine i) resonant frequency ii) Q-factor and iii) half power frequencies. Derive the necessary relation you use. (12)

- B) In the network shown in Fig.8, find the value of C for resonance to take place when $\omega=500\text{rad/s}$. Determine the branch currents. (8)


B. ETCE 2ND YEAR 1ST SEMESTER EXAMINATION, 2021
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

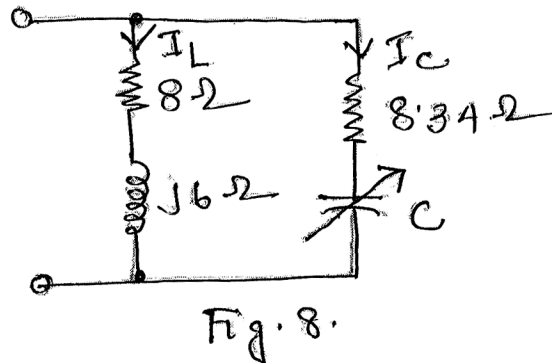


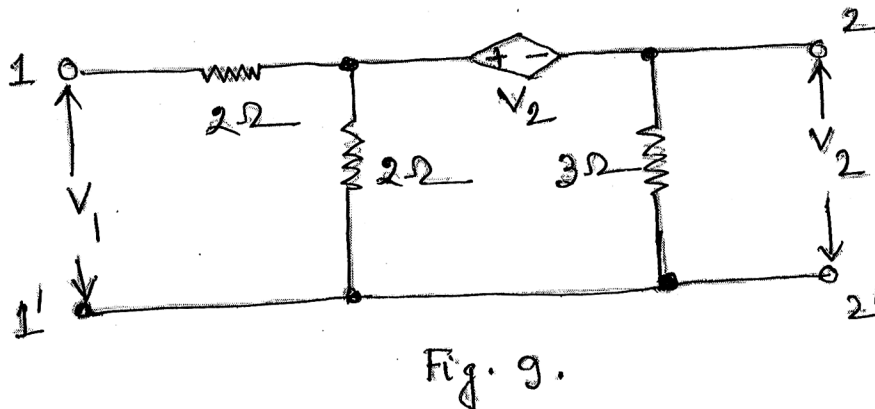- 6) A) Determine the Y and Z- parameters of the network shown in Fig.9 (13)



B) Design a composite low-pass filter to be terminated in 600Ω . It must have a cut-off frequency of 1kHz with very high attenuation at 1050Hz , 1250Hz and infinity. Draw the complete composite low-pass T-section. (7)

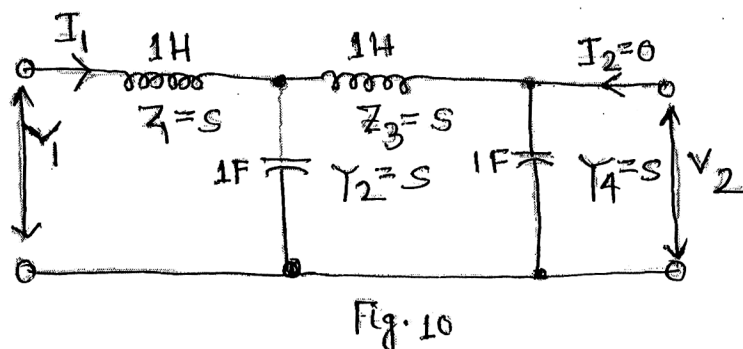- 7) A) Write the driving-point impedance of the ladder network in Fig.10. (10)



B. ETCE 2ND YEAR 1ST SEMESTER EXAMINATION, 2021
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

B) Find the function V_0/V_{IN} for the circuit shown in Fig.11. (10)

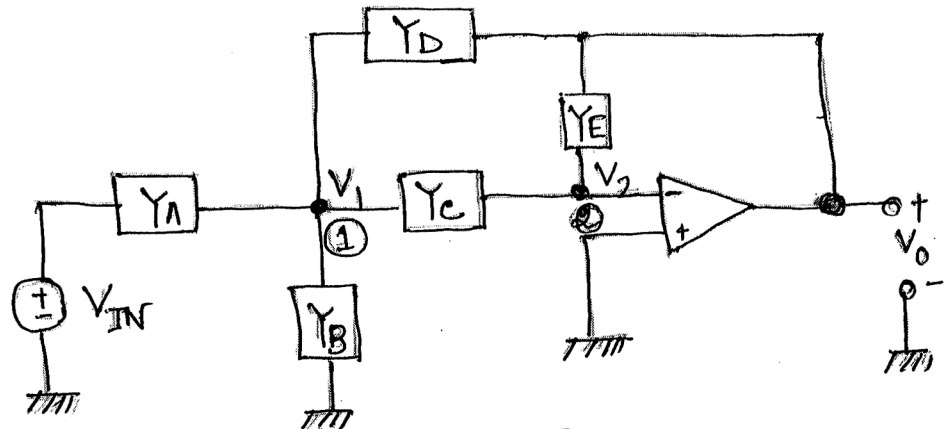


Fig. 11

- 8) A) Synthesize first and second Foster and Cauer forms of the LC driving point impedance function

$$Z_D(s) = \frac{(s^2+1)(s^2+16)}{s(s^2+4)} \quad (10)$$

- B) Synthesize the Foster I and II forms of the R-C driving point function

$$Z_D(s) = \frac{2s^2+12s+16}{s^2+s+3} \quad (10)$$

- 9) Write short note: (Any Four): 4×5

- i. PRF
- ii. LC driving point impedance function
- iii. Maximum power transfer theorem
- iv. Passive and active filters
- v. Fourier and Laplace transforms
- vi. Source transformation
- vii. Series and Parallel RLC circuits
- viii. Node and mesh analysis.