

**BACHELOR OF ELECTRONICS AND TELE-COMMUNICATION ENGINEERING**  
**THIRD YEAR FIRST SEMESTER SUPPLEMENTARY EXAMINATION, 2024**

**Analog CMOS Design and Technology**

TIME: 3 HOURS

FULL MARKS: 100



Answer ALL the four Segments below  
 (All parts of the same question must be answered together)

*Any approximation used in solving problems need to be properly justified*


**SEGMENT – I (Answer any ONE question)**

[CO1]

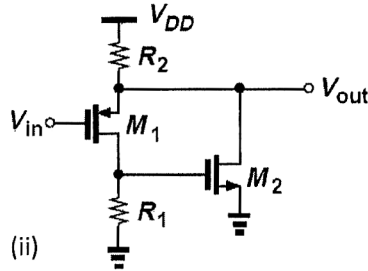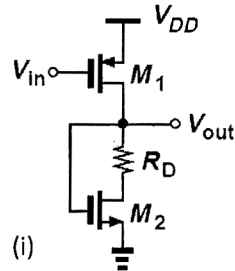- Q1.a) Discuss the effect of the following on the threshold voltage of a MOSFET: (i) increase in substrate doping density, (ii) increase of ambient temperature, and (iii) reduction of gate-oxide thickness. 6
- b) Compare the various performance aspects of BJT and MOSFET? 4
- c) Construct the low-frequency small-signal model of the following circuits (i) and (ii). Consider  $\lambda \neq 0$  and  $\eta = 0$ . 10



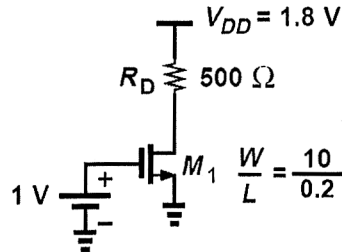- Q2.a) Draw the small-signal model of MOSFET including the internal capacitances. 5
- b) For the following circuit, determine the minimum possible value of the supply voltage so as to keep the transistor in saturation region. Assume  $\lambda = 0$ ,  $\mu_n C_{ox} = 250 \mu\text{A}/\text{V}^2$ , and  $V_{TH} = 0.6 \text{ V}$ . 5




[ Turn over

- c) Derive the small-signal expressions of (i) transconductance and (ii) output resistance of a common-source amplifier with source degeneration. Do not neglect channel-length modulation and body effect. 10


SEGMENT – II (*Answer any TWO questions*)

[CO2]

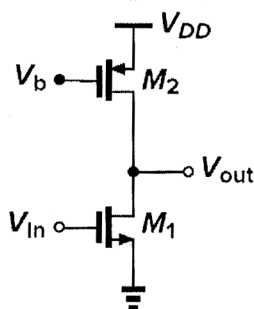- Q3.a) Draw and briefly discuss the advantages of a cascode structure. 5
- b) Considering both *thermal* and *flicker* noise, derive the expression of the output voltage noise spectrum for the following common-source amplifier. Hence find the rms noise voltage referred to the input terminal. 10




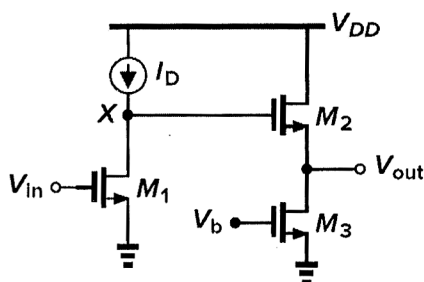- c) Discuss how distortion and noise are generated in an analog circuit. 5
- Q4.a) Draw a representative layout for ensuring matching in a 1:4 current mirror, clearly indicating the MOSFET terminals and the different layers as utilized. 10
- b) For the following circuit, derive expressions of: (i) low-frequency voltage gain (for  $\lambda$  and  $\eta \neq 0$ ), (ii) permissible minimum level of voltage swing at the node X, and (iii) maximum tolerable swing of  $V_{out}$ . 10



- Q5.a) Discuss on the input referred offset of an opamp. 4
- b) Draw the topology of a Telescopic cascode opamp. 4

- c) For the following amplifier, quiescent current = 0.25 mA,  $(W/L)_1 = (W/L)_2 = 30$ , and  $(W/L)_3 = (W/L)_4 = 50$ . Given,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2 = 2\mu_p C_{ox}$ ,  $\lambda_n = 0.1 \text{ V}^{-1}$ ,  $\lambda_p = 0.15 \text{ V}^{-1}$ , and  $V_{THn} = 0.5 \text{ V} = |V_{THp}|$ . Calculate the (i) voltage gain and (ii) maximum permissible voltage swing supported at the output. 12

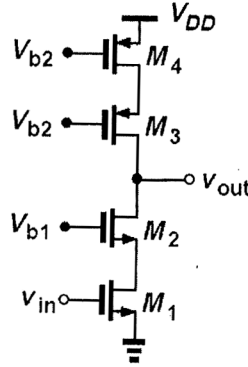

SEGMENT – III (Answer any ONE question)


[CO3]

- Q6.a) Describe the various steps of photolithography. 10
- b) Discuss the important steps involved in a typical CMOS process flow for fabricating NMOS and PMOS FETs on wafer, with representative schematics. 10
- Q7.a) Explain the short channel effect of *velocity saturation*. 10
- b) Discuss two commonly used methods for the doping of semiconductors. 10

SEGMENT – IV (Answer any ONE question)


[CO4]

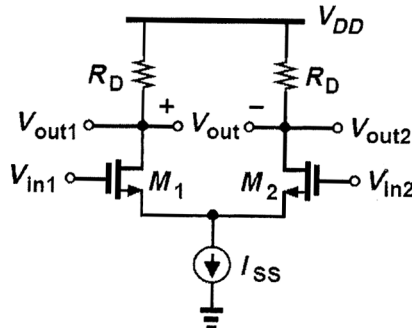- Q8.a) (i) Design the diff-amp for a power consumption of 4 mW and  $V_{OV}$  of 100 mV. (ii) For input common-mode of 1 V, find the value of  $R_D$  to place  $M_1$  and  $M_2$  at the edge of saturation. (iii) Find the voltage gain obtained from the resulting design. Assume  $V_{DD} = 2 \text{ V}$ ,  $\mu_n C_{ox} = 300 \mu\text{A/V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ ,  $\lambda = 0$  and  $\eta = 0$ . 12



- b) If a fabrication induced mismatch of 5% occurs between the two  $R_D$  resistances in the above circuit, derive the (i) expression and (ii) value of resulting CMRR. Consider that the current sink  $I_{SS}$  is realized by a suitably biased NMOSFET having  $\lambda_n = 0.1 \text{ V}^{-1}$ . 8

- Q9.a) Find the values (in Hz) of 3-dB BW and GBW of the below OTA. Given  $V_{DD} = 2 \text{ V}$ ,  $V_{THn} = 0.5 \text{ V} = |V_{THp}|$ ,  $\mu_n C_{ox} = 200 \mu\text{A/V}^2 = 2\mu_p C_{ox}$ , and  $\lambda_n = 0.1 \text{ V}^{-1} = 0.5\lambda_p$ . Also,  $(W/L)_{1,2} = 20$ ,  $(W/L)_{3,4} = 40$ ,  $C_L = 3 \text{ pF}$  and  $I_0 = 0.2 \text{ mA}$ . 10

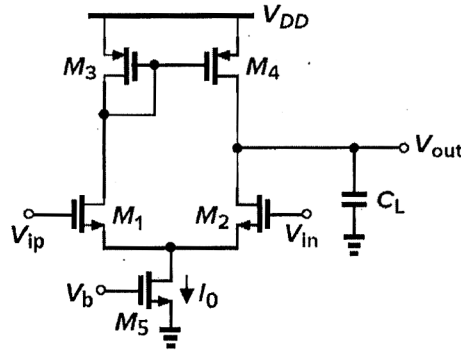

- b) Determine the expressions and values of the input common mode range (both ICMR<sub>+</sub> and ICMR<sub>-</sub>) of the above amplifier. Consider  $V_{OV,5} = 100 \text{ mV}$ . 10