

**BACHELOR OF ELECTRONICS AND TELE-COMMUNICATION ENGINEERING**  
**THIRD YEAR FIRST SEMESTER EXAMINATION, 2024**

**Analog CMOS Design and Technology**

TIME: 3 HOURS



FULL MARKS: 100

Answer ALL the four Segments below  
 (All parts of the same question must be answered together)


*Any approximation used in solving problems need to be properly justified*

**SEGMENT – I (Answer any ONE question)**

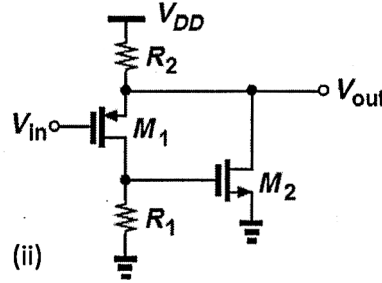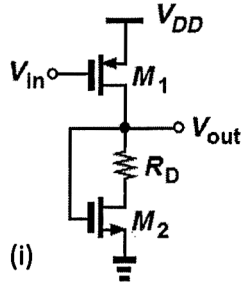- Q1.a) For long-channel MOSFET, discuss what happens to the threshold voltage if (i) substrate doping density is reduced, (ii) ambient temperature increases, and (iii) gate-oxide thickness is increased? 6
- b) Discuss what is *body-effect* in an N-MOSFET? 4
- c) Construct the low-frequency small-signal model of the following circuits (i) and (ii). Consider  $\lambda \neq 0$  and  $\eta = 0$ . 10



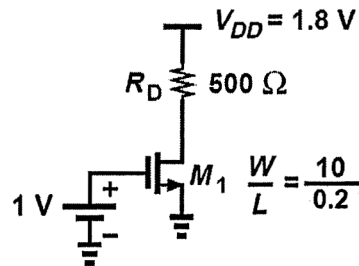- Q2.a) Describe the different internal capacitances within MOSFET using a schematic. 5
- b) For the following circuit, determine the minimum possible value of the supply voltage so as to keep the transistor in saturation region. Assume  $\lambda = 0$ ,  $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ , and  $V_{TH} = 0.5 \text{ V}$ . 5




[ Turn over


- c) Derive the small-signal expressions of (i) transconductance and (ii) output resistance of a common-source amplifier with source degeneration. Do not neglect channel-length modulation and body effect. 10

**SEGMENT – II (Answer any TWO questions)**

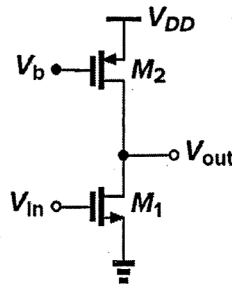- Q3.a) Briefly discuss on the origin of *distortion* and *noise* in an analog circuit. 5
- b) Considering both *thermal* and *flicker* noise, derive the expression of the output voltage noise spectrum for the following common-source amplifier. Hence find the rms noise voltage referred to the input terminal. 10




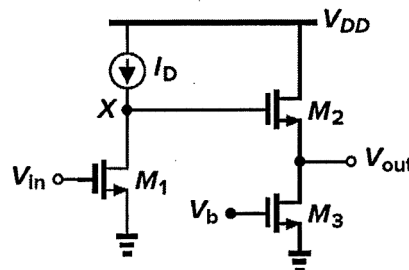- c) What is  $1/f$  corner frequency? In the above circuit, if the width and length are increased by 2x for both the transistors (i.e., keeping aspect ratio unchanged), explain how the corner frequency might change. 5
- Q4.a) Discuss how the matching of MOS transistors may be realized in IC fabrication, together with the necessity for the same. 4
- b) From the above perspective, draw a representative layout of 1:4 current mirror, clearly indicating the MOSFET terminals and the different layers as utilized. 6
- c) For the following circuit, derive expressions of: (i) low-frequency voltage gain (for  $\lambda$  and  $\eta \neq 0$ ), (ii) permissible minimum level of voltage swing at the node X, and (iii) maximum tolerable swing of  $V_{out}$ . 10



- Q5.a) Explain the advantages of differential signaling in an integrated circuit. 4
- b) Define and derive the expression of *slew-rate* of a 5-transistor OTA. 4

- c) For the following amplifier, quiescent current = 0.5 mA,  $(W/L)_1 = (W/L)_2 = 30$ , and  $(W/L)_3 = (W/L)_4 = 40$ . Given,  $\mu_n C_{ox} = 100 \mu A/V^2 = 2\mu_p C_{ox}$ ,  $\lambda_n = 0.1 V^{-1}$ ,  $\lambda_p = 0.15 V^{-1}$ , and  $V_{THn} = 0.5 V = |V_{THp}|$ . Calculate the (i) voltage gain and (ii) maximum permissible voltage swing supported at the output. 12

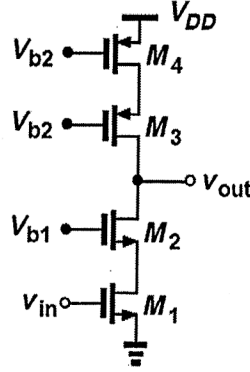


**SEGMENT – III (Answer any ONE question)**

- Q6.a) Describe the various uses of  $SiO_2$  in CMOS technology with suitable diagram. 5
- b) Discuss two common techniques of doping in semiconductor fabrication. 5
- c) Indicate the important steps involved in a typical CMOS process flow with representative schematics. 10
- Q7.a) Explain *drain-induced barrier lowering* with proper diagram. 10
- b) Describe the various steps of photolithography. Discuss about its challenges in lower technology nodes. 10


**SEGMENT – IV (Answer any ONE question)**

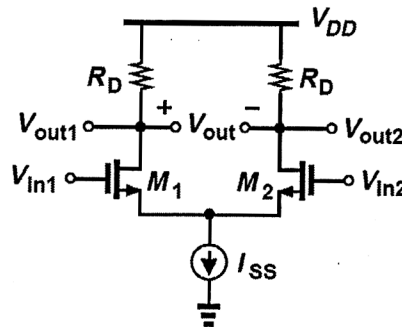- Q8.a) (i) Design the diff-amp for a power consumption of 2 mW and  $V_{OV}$  of 100 mV. (ii) For input common-mode of 1 V, find the value of  $R_D$  to place  $M_1$  and  $M_2$  at the edge of saturation. (iii) Find the voltage gain obtained from the resulting design. Assume  $V_{DD} = 2 V$ ,  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $V_{TH} = 0.5 V$ ,  $\lambda = 0$  and  $\eta = 0$ . 12



- b) If a fabrication induced mismatch of 5% occurs between the two  $R_D$  resistances in the above circuit, derive the (i) expression and (ii) value of resulting CMRR. Consider that the current sink  $I_{SS}$  is realized by a suitably biased NMOSFET having  $\lambda_n = 0.1 \text{ V}^{-1}$ . 8

- Q9.a) Find the values (in Hz) of 3-dB BW and GBW of the below OTA. Given  $V_{DD} = 1.8 \text{ V}$ ,  $V_{THn} = 0.5 \text{ V} = |V_{THp}|$ ,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2 = 2\mu_p C_{ox}$ , and  $\lambda_n = 0.1 \text{ V}^{-1} = 0.5\lambda_p$ . Also,  $(W/L)_{1,2} = 20$ ,  $(W/L)_{3,4} = 40$ ,  $C_L = 3 \text{ pF}$  and  $I_0 = 0.2 \text{ mA}$ . 8

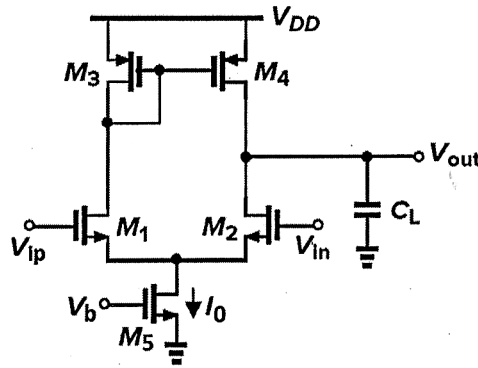

- b) Determine the expressions and values of the input common mode range (both  $\text{ICMR}_+$  and  $\text{ICMR}_-$ ) of the above amplifier. Consider  $V_{OV,5} = 100 \text{ mV}$ . 7
- c) Discuss how frequency compensation is done for ensuring stability of a two-stage OTA in negative feedback. 5