

**B. INS. & ELEC. ENGINEERING 2<sup>ND</sup> YEAR 1<sup>ST</sup> SEMESTER EXAMINATION 2024**

**ELECTRONIC CIRCUITS**

**TIME: 3 HOURS**

**FULL MARKS: 100**

**List of Course Outcomes (CO):**

CO1: Classify and analyze different types of diode circuits (K2, K4, A1)

CO2: Identify and interpret the importance of biasing in electronic amplifiers (K3, A1)

CO3: Describe and explain the behavior of small signal amplifiers (K2, A1)

CO4: Differentiate and examine feedback circuits of various kinds (K4, A2)

CO5: Explain and analyze the operation of oscillators (K2, K4, A1)

**Instructions to the Examinees:**

- Each module in the question paper matches up with the corresponding CO
  - Attempt **ALL** the questions from **ALL** the modules for the attainment of all the Cos
  - Alternative questions (if any) exist within a module, not across the modules
  - Different parts of same question should be answered together
- 

[ Turn over

**MODULE 1**

ATTEMPT ANY TWO QUESTIONS FROM THIS MODULE

1.

- (a) Draw the transfer characteristics of an ideal diode. Hence, find out its resistances in different regions of operations.
- (b) Find out the output waveform of the circuit shown in Fig. 1. Assume the RC time constant is much greater than the period of the signal.

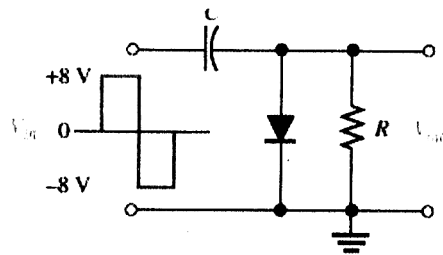


Fig. 1

4+6

2.

- (a) In a half-wave rectifier, what will happen if the diode is short-circuited?
- (b) Why do we prefer centre-tap circuit to bridge circuit in low voltage applications?
- (c) Discuss the importance of PIV in rectifier service.
- (d) What type of filter circuit is used after rectification? Why is it used?
- (e) Draw the diagram of a negative clipper circuit.

2X5

3.

- (a) Design a generic circuit of a voltage regulator and explain its operation briefly.
- (b) The voltage regulator is to power a car radio at  $V_L = 9\text{ V}$  from an automobile battery whose voltage may vary between 11 and 13.6 V. The current in the radio will vary between 0 (off) to 100 mA (full volume). Calculate the value of the current limiting series resistance. Assume that the minimum zener current to be one-tenth of the maximum zener current.

3+7

**MODULE 2****ATTEMPT ANY THREE PARTS FROM Q. NO. 4**

- (a) Calculate the terminal voltages of the BJT in Fig. 2.

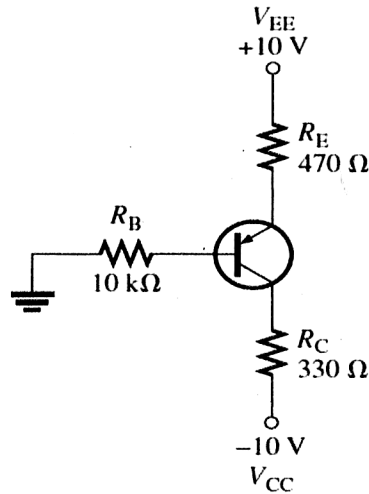


Fig. 2

- (b) The circuit in Fig. 3 is subjected to a temperature variation from  $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$ . The dc current gain decreases by 50 percent at  $0^{\circ}\text{C}$  and increases by 75 percent at  $70^{\circ}\text{C}$  from its nominal value of 110 at  $25^{\circ}\text{C}$ . What are the changes in collector current and collector to emitter voltage over the temperature range of  $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$ ?

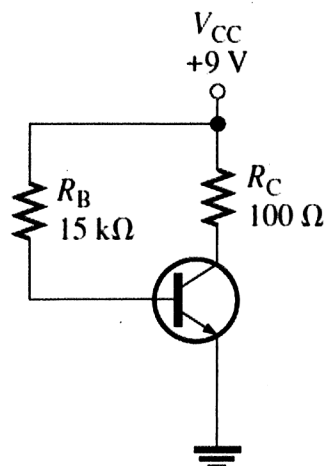


Fig. 3

- (c) How can an amplifier circuit with un-bypassed emitter resistor increase the stability? Discuss in light of the notion of feedback.
- (d) What is the difference between stiff and non-stiff voltage divider bias? Explain.

3X5

### MODULE 3

#### ATTEMPT Q. NO. 5 AND ANY ONE FROM THE REST

5. For the common emitter amplifier shown in Fig. 4, calculate the mid-band gain and 3-dB bandwidth using appropriate graph paper. The transistor's datasheet provides the following:  $\beta_{dc} = \beta_{ac} = 100$ ,  $V_A = \infty$ ,  $c_\pi = 10 \text{ pF}$ ,  $c_\mu = 1.5 \text{ pF}$ . Consider appropriate number of frequency points both in the low and high frequency range in drawing the frequency response. Assume  $V_T = 25 \text{ mV}$ .

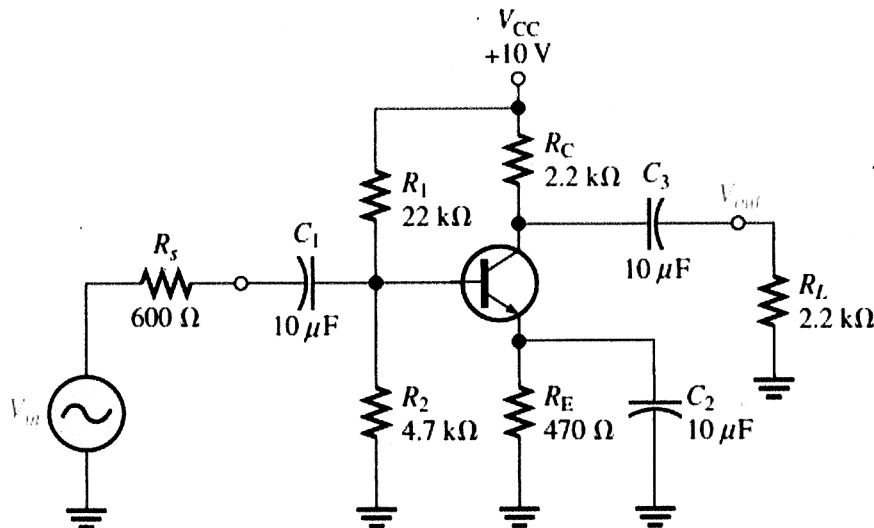


Fig. 4

35

- 6.
- (a) Under which condition, will the slope of AC and DC load line be identical?
- (b) Draw one amplifier circuit for which voltage gain remains insensitive to the temperature of the ambience.
- (c) Which type of amplifier configuration is used just before the load in an audio amplifier? Justify your answer.
- (d) What is the advantage of cascode amplifier over CE or CB amplifier alone?

2+3+2+3

7.

- (a) What do you understand by differential signal?
- (b) Draw one differential amplifier circuit and calculate the expression of differential voltage gain. Establish the same using half-circuit concept as well.

2+(6+2)

#### MODULE 4

ATTEMPT ANY ONE QUESTION FROM THIS MODULE

8.

- (a) Why is it not possible to realize current-shunt feedback using single stage CE amplifier?
- (b) Draw the schematic diagram of a feedback amplifier which exhibits current-shunt feedback. Hence calculate the expression of input and output resistance.

2+(4+4)

- 9. Draw the circuit diagram of a voltage-series feedback amplifier. Hence calculate the expression of voltage gain with & without feedback and feedback factor.

10

#### MODULE 5

ATTEMPT ANY ONE QUESTION FROM THIS MODULE

- 10. Draw and explain the operation of an RC phase-shift oscillator circuit. Show that the circuit will oscillate at a frequency of  $f_0 = \frac{1}{2\pi\sqrt{6}RC}$ . Find out the value of the closed-loop gain for sustained oscillation.

10

11.

- (a) Draw the generic LC oscillator circuit and hence derive the condition for oscillation.
- (b) From the generic oscillation criterion, synthesize Colpitts oscillator circuit.

7+3