

**B. INS. & ELEC. ENGINEERING 3<sup>RD</sup> YEAR 2<sup>ND</sup> SEMESTER EXAMINATION 2024**

**ANALOG MOS CIRCUIT DESIGN**

**TIME: 3 HOURS**

**FULL MARKS: 100**

**List of Course Outcomes (CO):**

CO1: Classify and analyze different types of MOS amplifiers (K4, A1-recognize)

CO2: Explain and interpret the importance of differential amplifiers (K3, A1)

CO3: Describe and explain the behavior of current mirrors (K2, A1)

CO4: Explain and analyze the frequency response of MOS amplifiers (K4, A1)

**Instructions to the Examinees:**

- Each module is mapped with the corresponding CO
- Attempt questions from **ALL** the modules
- Alternative questions exist within a module, not across the modules
- Different parts of same question should be answered together
- Clearly state any assumption and derive the necessary equation(s) for calculation
- Unless otherwise stated, use the device data shown in Table I and assume  $V_{DD} = 3\text{ V}$  where necessary

Table I

Symbol	Value	Unit
$V_{th,n}$	0.7	V
$V_{th,p}$	-0.8	V
$\gamma_n$	0.45	$V^{1/2}$
$\gamma_p$	0.4	$V^{1/2}$
$\mu_n C_{ox}$	50	$\mu A/V^2$
$\mu_p C_{ox}$	25	$\mu A/V^2$
$\lambda_n$	0.1	$V^{-1}$
$\lambda_p$	0.2	$V^{-1}$

-----

[ Turn over

**MODULE 1**

(ATTEMPT ALL QUESTIONS FROM THIS MODULE)

1. Sketch  $I_X$  and trans-conductance of the transistor as a function of  $V_X$  for any one of the circuits in Fig. 1 as  $V_X$  varies from 0 to  $V_{DD}$ .

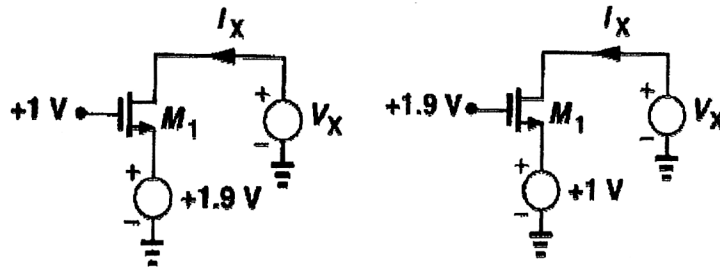


Fig. 1

10

2. Sketch  $v_{out}$  versus  $v_{in}$  for any one of the circuits in Fig. 2 as  $v_{in}$  varies from 0 to  $V_{DD}$ . Identify the important transition points.

 


Fig. 2

10

3. Assuming all MOSFETs are in saturation, calculate the small signal voltage gain for any one of the circuits in Fig. 3. ( $\lambda \neq 0$ ,  $\gamma = 0$ )

 


Fig. 3

10

4. Suppose in the source follower of Fig. 4(a),  $\left(\frac{W}{L}\right)_1 = 40$ ,  $I_1 = 200 \mu A$ ,  $V_{th,0} = 0.6 V$ ,  $2\phi_F = 0.7 V$ . Calculate  $v_{out}$  for  $v_{in} = 1.2 V$ . If  $I_1$  is implemented as  $M_2$  in Fig. 4(b), find the minimum value of  $\left(\frac{W}{L}\right)_2$  for which  $M_2$  remains saturated.

 


Fig. 4

10

## MODULE 2

(ATTEMPT Q. NO. 5 AND ANY ONE FROM THE REST)

5. A differential pair uses input NMOS devices with  $\left(\frac{W}{L}\right) = 100$  and a tail current of 1 mA. What is the equilibrium overdrive voltage of each transistor? How is the tail current shared between the two sides if  $V_{in,1} - V_{in,2} = 50 mV$ ? What is the equivalent  $G_m$  under this condition? Assume  $\left(\frac{W}{L}\right) = 100$  and tail current of 1 mA.

10

6. What is the significance of CMRR? Calculate the value of CMRR of an asymmetric differential amplifier stage with non-ideal tail current source.

3+12

7. Assuming the circuit shown in Fig. 5 is symmetric, sketch  $V_{out}$  as  $V_{in,1}$  and  $V_{in,2}$  are (i) equal and vary from zero to  $V_{DD}$  & (ii) vary differentially from zero to  $V_{DD}$

 


Fig. 5

15

**MODULE 3**

(ATTEMPT Q. No. 8 AND ANY TWO FROM THE REST)

8. Select **one or more** correct option(s) from the choices given below:

- (a) Current mirror circuits can be constructed using
  - (i) n-MOS only
  - (ii) p-MOS only
  - (iii) Both n-MOS and p-MOS in the same circuit
  - (iv) Both n-MOS and p-MOS in different circuits
- (b) Cascode current mirror circuit is used to
  - (i) Suppress the effect of channel length modulation
  - (ii) Improve the voltage headroom
  - (iii) Minimize the requirement of MOS transistors
  - (iv) Reduce the power consumption
- (c) Active current mirrors are those which
  - (i) Carry bias current only
  - (ii) Carry time varying current
  - (iii) Do not carry any current through it
  - (iv) None of the above

5

9. Assuming perfect symmetry, sketch the output voltage of the circuit in Fig. 6 as  $V_{DD}$  varies from 3 V to 0. Assume that for  $V_{DD} = 3$  V, all of the devices are saturated.

 


Fig. 6

10

10. Assuming all the transistors are identical, sketch  $V_X$  and  $V_Y$  as a function of  $V_{DD}$  for the circuit in Fig. 7.

 


Fig. 7

10

11. Show that the common-mode gain of the circuit in Fig. 8 with  $g_m$  mismatch is approximately given by:

$$\frac{\Delta V_{out}}{\Delta V_{in,CM}} \approx \frac{(g_{m1} - g_{m2})r_{o3} - \left(\frac{g_{m2}}{g_{m3}}\right)}{1 + (g_{m1} + g_{m2})R_{SS}}$$

 


Fig. 8

10

MODULE 4

12. Calculate the input impedance of any one of the circuits in Fig. 9.

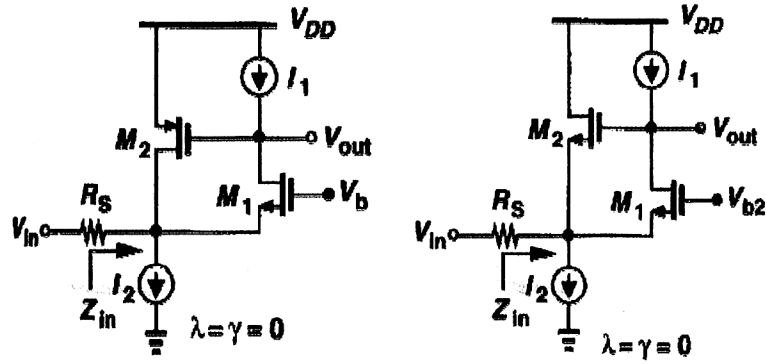


Fig. 9