

**B.E. MECHANICAL ENGINEERING FIRST YEAR FIRST SEMESTER
SUPPLEMENTARY EXAM - 2024**

ELECTRONICS

Time : 3 hrs

Full Marks: 100

Answer any five questions.

1. Draw the block diagram of a zero-crossing detector and explain the functions of individual blocks. 20
2. a) Explain the operation of a positive diode clipper circuit. 10
b) Discuss cutoff, active and saturation states of a transistor. 10
3. a) Explain with a circuit diagram the use of a zener diode as a voltage regulator. 10
b) Draw any transistor biasing circuit, find its Q-point and plot it on the load line. 10
4. a) Draw the circuit diagram of a half wave rectifier and explain its operation. 10
b) An amplifier has an open-circuit voltage gain of 5, an input resistance of $1\text{ k}\Omega$, and an output resistance of $10\ \Omega$. The amplifier is connected to a sinusoidal voltage source of 1 V rms , which has an output resistance of $100\ \Omega$, and to a load resistance of $50\ \Omega$. What will be the rms value of the output voltage? 10
5. a) Draw the circuit diagram of a practical CE amplifier and obtain the expression for the voltage gain and the input impedance. 12

b) Draw the circuit diagram of an OP AMP non-inverting amplifier and derive the expression for the voltage gain. 8

6. Write notes on the following: 4x5=20

- (a) Sensors and Actuators
- (b) Ripple factor and Rectification efficiency
- (c) Op-amp voltage follower
- (d) Frequency response of an amplifier

7. a) Obtain the truth table for the following function: $f = A + BC$ 6

b) Implement the following logic function using MOS transistors: $f = AB + C$ 6

c) Implement the following Boolean function using (i) only NAND gates and (ii) only NOR gates: $f = AB + C$ 8

8. a) Express the following function in minterm and maxterm forms. 10

$$f(A,B,C) = (A + B) C$$

b) Simplify the following Boolean function using K-map. 10

$$f(A,B,C,D) = \Sigma(0, 1, 3, 7, 8, 9, 11, 15)$$