

B. POWER ENGINEERING EXAMINATION -2024

(2nd Year – 1st Semester)

SUBJECT – Circuit Theory

Time: Three hours

Full Marks: 100


Answer any *five* questions as directed under each group

Assume suitable value for missing data, if any

All the values of resistors are in Ω .**All parts of a question to be answered at one place.**

No. of Question		Marks
	<p style="text-align: center;">Group A</p> <p style="text-align: center;">Answer any one questions</p>	
1.(a)	State and prove Maximum Power Transfer Theorem with suitable example.	6
(b)	<p>In the circuit shown below, $E_1 = 240V$, (i) If $E_2 = 50V$, find the value of R_L which results in maximum power absorbed in it and the corresponding maximum power (ii) If E_2 is variable, what should be its value to limit the maximum dissipation in R_L to 10 W?</p>	14
2. (a)	What is a supermesh? Explain the techniques for the solution of networks having supermesh with suitable example.	8
(b)	For the network as shown below, determine the current flowing through the 6Ω resistor.	12

[Turn over

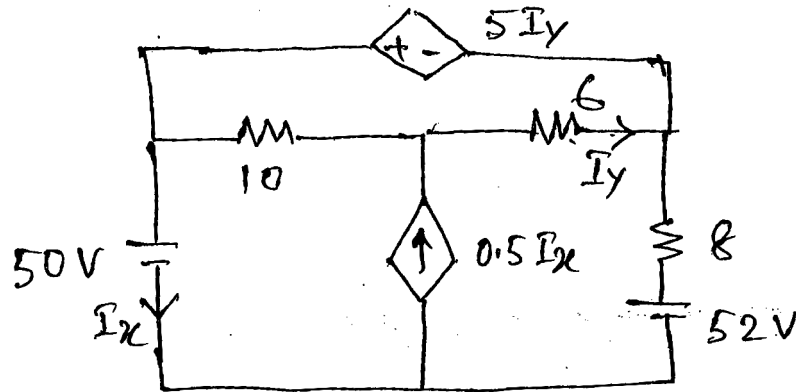

Group B
Answer *any one* question

3. (a) Define and explain the following with suitable examples:

4+3+3

- (i) Cut set and fundamental cut set matrix
- (ii) Tie set matrix
- (iii) Incident matrix


(b) The incidence matrix of a directed graph is shown below. Draw the directed graph. Select a particular tree of your choice and write down the fundamental cut set matrix for the same.

10

$$[A] = \begin{bmatrix} 0 & 1 & 0 & 1 & -1 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 0 & -1 \\ -1 & -1 & -1 & 0 & 1 & 1 & 0 & 0 \\ 1 & 0 & 0 & -1 & 0 & 0 & 1 & 1 \end{bmatrix}$$

4. For the network as shown below, draw the directed graph and write down the reduced incidence matrix. Use it to determine the branch voltages.


20

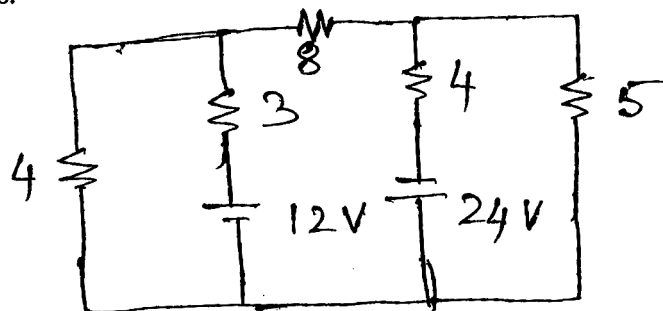

Group C

Answer **any one** question

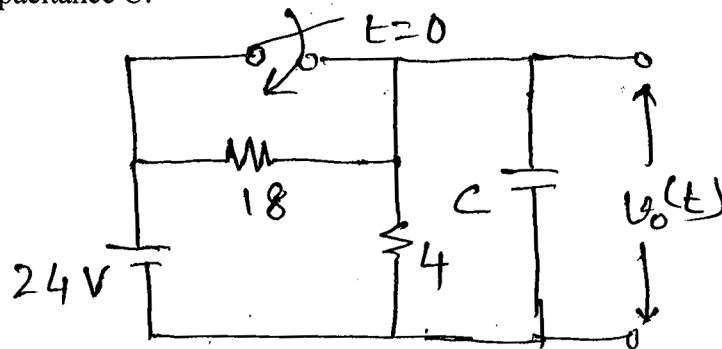
5. (a) Find the response current of a series RLC circuit with $R = 5 \Omega$, $L = 1 H$ and $C = 0.25 F$ when each of the following driving force is applied. (i) $12 r(t-2)$ and (ii) $3 u(t-3)$ 10
- (b) A pulse of width b and magnitude $10 V$ is applied at time t to a series RC circuit with $R = 1.0 \Omega$ and $C = 0.25 F$. Find current flowing through the circuit assuming zero net charge across the capacitor. 10
6. Consider the circuit as shown in below. The input to the circuit is $24 V$. The output of the circuit, the voltage across the capacitor, is given to be $v_o(t) = 16 - 12e^{-0.6t} V$ when $t > 0$. Determine the value of the capacitance C . 20





Group D

Answer **any one** question

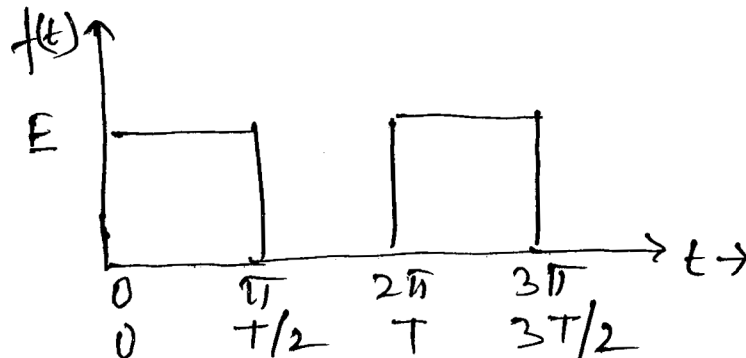7. Determine the Fourier Series for the following waveform and plot the magnitude spectrum. 20



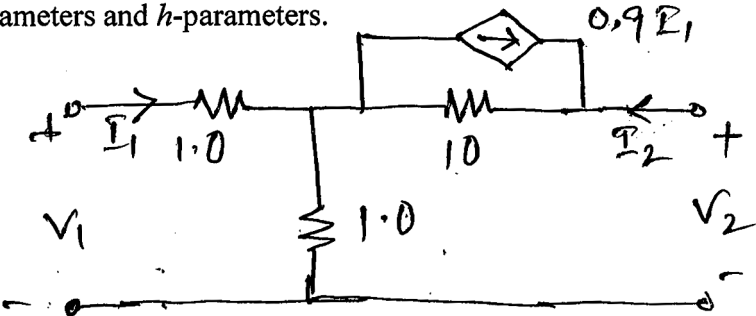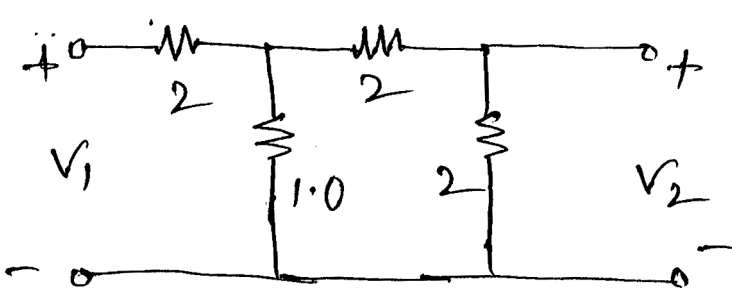8.	<p>Determine the two parameters, power consumed by the circuit and the power factor of the circuit whose expression for the voltage and currents are as follows:</p> $v(t) = 269 \sin(314t + 10^\circ) + 79 \sin(942t + 48^\circ)$ $i(t) = 19.8 \sin(314t - 47^\circ) + 2.2257 \sin(942t - 29.7^\circ)$	20
	<p style="text-align: center;">Group E Answer <i>any one</i> question</p> <p>(9) Find the Z-parameters for the network shown below. Hence find Y-parameters and h-parameters.</p> 	20
10.	<p>Two identical sections of the network as shown below are connected in cascade. Obtain the transmission (ABCD) overall network.</p> 	20