MASTER OF ELECTRONICS AND TELE-COMMUNICATION ENGINEERING/ ELECTRICAL ENGINEERING/CONTROL SYSTEM ENGINEERING/BIOMEDICAL ENGINEERING FIRST YEAR SECOND SEMESTER – 2024

Embedded Systems

Time: 3 hours Full Marks: 100

Answer any 4 questions.

- 1. An output pulse z is to be coincident with the second x_2 pulse, immediately following an x_1 pulse. Design the sequential state machine. [25]
- 2. Design an ASIC for a Fibonacci Sequence Generator. Draw and explain the data-flow path, IC signal pins and the complete logic diagram. [25]
- 3. a) What is a hierarchical state machine?
- b) Design the state diagram of a hierarchical state machine of an elevator. Consider power failure and recovery and fire-extinguishing cases in your hierarchical design. [5+20]
- 4. a) Using at least 3 states, construct a stochastic automaton to recognize the sequence abb.
 - b) Show the problem of evaluation of the above sequence with presumed probabilities.
 - c) Realize the same by a fuzzy automaton.
 - d) Realize (a) by lattice automaton, and evaluate the lattice belief to recognize *abb* for a given lattice/ Hasse diagram. Show the Hasse diagram. [7+6+6+6]
- 5. a) Develop a PLA to store 01 at address 101, 10 at address 110, and 11 at address 111.
 - b) Write the outputs y_1 , y_0 as a function of input address $a_2a_1a_0$.
 - c) What is a PLD? Modify the equivalent PAL of the given PLA into a PLD. What is the logic function that the PLD realizes?
 - d) Show how will you realize Half-adder on a Fairchild Corporation's p-ASIC architecture?

[7+3+10+5]

- 6. a) Draw and explain the schematic architecture of Arm Processor.
 - b) Show the steps of computation of the instruction ADD r_0 , r_1 , $[r_2]$ and demonstrate the data and address flow paths inside the processor.
 - c) What is the importance of the process statement in VHDL programming? Explain why and how the process statement is used to avoid glitch in a digital circuit. [8+5+12]

- 7. a) Draw and explain the functional block diagram of a dot-matrix printer.
 - b) Develop an interface between a dot-matrix printer and 8085A based micro-computer system to transfer 10 bytes of data to the printer from the system buffer.
 - c) Also construct an assembly-level program to realize part (b).

[10+5+10]

- 8. a) State the principle of interrupt masking in an 8085 microprocessor using the I-register.
 - b) Develop an assembly level program to change the set-point in a process control loop under online condition (i.e., without shutting down the process) using nested interrupt handling. The user is supposed to press the following key sequence: Vector Interrupt, 5, 2 to describe the updated set-point as 52 decimal in a given memory location (say 2080H) reserved for set-point storage.

 [5+20]