

M.TECH. IN ILLUMINATION TECHNOLOGY & DESIGN EXAMINATION, 2024
(1st Year, 2nd Semester)

RENEWABLE ENERGY BASED LIGHTING SYSTEM

Time: Three Hours

Full Marks: 100

Use a separate Answer-Script for each part
PART – II (50 marks)


Answer any three questions. Question no. 2 carries the highest marks.

- | | | |
|--------------|---|----------|
| 1.(a) | How behavioral factors affects the selection of a battery. | 4 |
| (b) | What is memory effect in case of a rechargeable battery? | 3 |
| (c) | Name the electrodes used in Lead-acid battery. | 2 |
| (d) | A smart solar photovoltaic system has a 48V, 10 kAh Battery bank. The Charge controller cum inverter connected to the battery sets a float voltage of 52.8V at the normal ambient temperature (27° C). Calculate the float voltages required for incorporating the temperature compensation in the charge controller when the battery will be used in Jaisalmer during the summer (52° C) and in Pahalgam during winter (-25°C). According to the manufacturer the compensation required is -3.6 mV/°C/cell. | 7 |
| 2.(a) | Any discharge lamp has negative resistance characteristics – justify. | 3 |
| (b) | What type of problem does a discharge lamp face due to this type of characteristics? | 3 |
| (c) | How the problem is overcome? | 3 |
| (d) | Discuss the operation of EM ballast of a florescent lamp. | 9 |
| 3.(a) | Draw the circuit diagram and explain the operation of a Boost Chopper | 8 |

[Turn over

- (b) A boost chopper has input voltage of 24V and output voltage of 48V. If the non-conducting time of the SCR is $150\mu\text{s}$ compute the pulse width of the output voltage. In case the pulse width is halved for constant frequency operation, find the new output voltage. 8

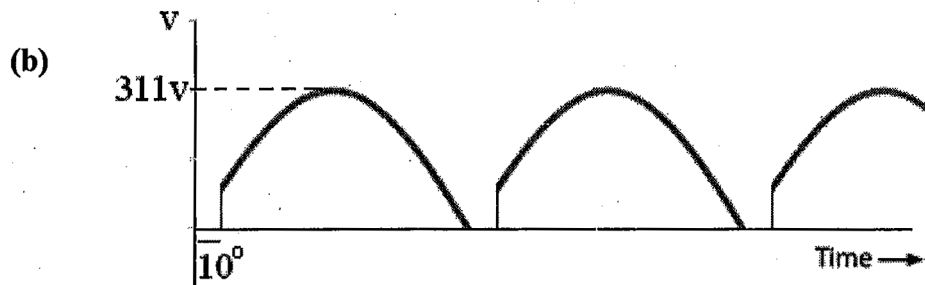4. (a) Derive the expression of output (DC) voltage of a single phase full controlled full-wave rectifier as a function of triggering angle. Draw the necessary waveforms also. 8



The voltage waveform from a SCR based dimming circuit is shown. What will be the power consumption of a 220V, 40W lamp (resistive) connected to this voltage? To reduce the power consumption by 20% what should be the triggering angle? 8

5. (a) At least two types of power electronic converters are required for the electronic ballast of any discharge lamp – justify 4
- (b) A DC-DC converter requires at least one inductor- justify 4
- (c) Write a short note on pulse width modulation (PWM) used for power converters. 8

Form A: Paper-setting Blank

Ref. No. Ex PG/IlluTD/T/122A/2024M Tech in Illumination Tech. & Design, 2nd sem **EXAMINATION, 20 24****(1st/2nd Semester/Repeat/Supplementary/Spl. Supplementary/Old/Annual/Bi-Annual)****SUBJECT** Renewable Energy based lighting Systems
(Name in full)**PAPER****Full Marks 30/ 100****(15/50 marks for each part)****Time : Two hours/Three hours/Four hours/Six hours****Use a separate Answer-Script for each part**

No. of questions	Part-I / Part II Answer any three from the following. Two marks for neatness.	Marks
Q1 a) b)	Write briefly about aerodynamics in case of wind turbine, with elaborations about Lift & Drag in case of a typical airfoil. Discuss the properties desired in semiconductors for solar cell use.	10+6
Q2 a) b)	With neat block diagram explain the operation of a solar PV system. Define the following term i) solidity ii) Tip speed ratio iii) Pitch	6+10
Q3 a) b)	Sketch the diagram of a HAWT and explain the functions of its main components. Explain the principle of wind energy conversion.	10+6
Q4 a) b)	With neat diagram explain the process of gasification in a Fluidized-Bed type gasifier. Derive the expression for power developed due to wind	8+8
Q5	Explain in details the following I) Down Draft Gasifier with neat diagram II) V-I and P-V Characteristic Solar Photo Voltaic System.	8+8