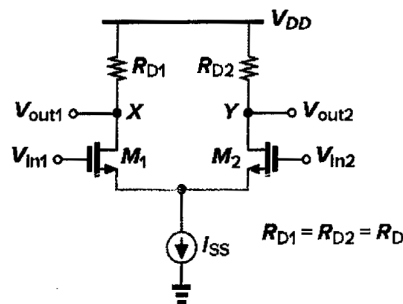


M.TECH. VLSI AND MICRO ELECTRONICS FIRST YEAR FIRST SEMESTER - 2024**Subject : ADVANCED ANALOG IC DESIGN****Time : 3 hours****Full Marks :100****Instructions : Answer any five questions and write answers of all parts of a question together**

1. a) Write the drain current expression and list the large signal model parameters of a long channel nMOSFET. [5]
 b) Explain channel length modulation. [5]
 c) Explain the change of threshold voltage with the application of body bias. [5]
 d) In a long channel nMOSFET calculate the threshold voltage when a body bias of 5V is applied.
 Given that $V_{FB}=0.2V$, $N_A=10^{17}/cc$, $t_{ox}=10nm$, $\epsilon_{Si}=11.9\epsilon_0$, $\epsilon_{ox}=3.9\epsilon_0$, $\epsilon_0=8.85 \times 10^{-12} F/m$. [5]
2. a) Draw and explain the MOS diode as an active resistor. Find the expression for the resistance offered. [5+5]
 b) Draw and explain the n-channel current mirror. Discuss three non-ideal effects that cause the current mirror deviate from the ideal situation. [4+6]
3. a) Explain the advantages of Differential amplifier over single ended amplifier. [5]
 b) Draw the block diagram of an OPAMP and briefly explain the function of each stage. [5]
 c) From the large signal analysis of the basic nMOS differential pair of below Fig. derive the expression for the differential voltage gain. [10]



4. a) List the requirements to design an OP-Amp. [5]
 b) Explain the large signal transconductance characteristics of a CMOS differential amplifier. [10]
 c) Draw a CMOS differential amplifier with current mirror load. Write the expression for ICMR. [5]
5. a) Explain Miller effect in common source amplifier. If the gate-drain capacitance is 1pF and gain of the amplifier is -50 then calculate the Miller capacitance at the input side of the amplifier. [3+2]
 b) Draw and explain Cascode Amplifier to avoid Miller effect. [10]
 c) Draw a simple Cascode amplifier with active load. How can it reduce the Miller effects? [2+3]
6. a) What are the advantages and disadvantages of BiCMOS over MOSFET and BJT. [5]
 b) Draw and calculate the composite transconductance of Darlington pair BiCMOS circuit. [2+5]
 c) Explain a BiCMOS current mirror. [8]
7. a) Discuss the primary advantages and disadvantages of switched capacitor circuits. [5]
 b) Design a resistance with the help of a switched capacitor. [10]
 c) For a parallel switched capacitor circuit of a resistor if clock frequency is 250KHz, $C_1=C_2=C$, find the value of capacitor to design a 1M Ω resistor. [5]